

ALTERNATING CURRENT WS 1

Class 12 - Physics

1. Mr. Iyer takes a grinder rated 220 V, 50 Hz to the U.S where supply is 110 V, 60 Hz. He needs to use a [1]
 - a) step-down transformer with turn ratio 2 : 1
 - b) step-up transformer with turn ratio 1 : 3
 - c) step-up transformer with turn ratio 1 : 2
 - d) step-down transformer with turn ratio 5 : 2

2. What is the ratio of inductive and capacitive reactance in an ac circuit? [1]
 - a) $\omega^2 LC$
 - b) LC^2
 - c) $\omega^2 L$
 - d) $\frac{LC}{\omega^2}$

3. When an alternating voltage $E = E_0 \sin \omega t$ is applied to a circuit, a current $I = I_0 \sin(\omega t + \frac{\pi}{2})$ flows through it. [1]
 The average power dissipated in the circuit is
 - a) $E_{\text{rms}} \cdot I_{\text{rms}}$
 - b) $\frac{E_0 I_0}{\sqrt{2}}$
 - c) Zero
 - d) $E_0 I_0$

4. A 15Ω resistor, an 80 mH inductor and a capacitor of capacitance C are connected in series with a 50 Hz ac source. If the source voltage and current in the circuit are in phase, then the value of capacitance is [1]
 - a) $100 \mu\text{F}$
 - b) $127 \mu\text{F}$
 - c) $160 \mu\text{F}$
 - d) $142 \mu\text{F}$

5. Alternating current can not be measured by d.c. ammeter, because: [1]
 - a) average value of current of complete cycle is zero
 - b) a.c. cannot pass through a.c. ammeter
 - c) a.c. ammeter will get damaged
 - d) a.c. changes direction

6. In a LCR-circuit, capacitance is changed from C to 2 C. For the resonant frequency to remain unchanged, the inductance should be changed from L to: [1]
 - a) $L/4$
 - b) $4 L$
 - c) $2 L$
 - d) $L/2$

7. In a transformer, number of turns in the primary is 140 and that in the secondary is 280. If current in primary is 4 A, then that in the secondary is: [1]
 - a) 6 A
 - b) 10 A
 - c) 2 A
 - d) 4 A

8. A 100 mH coil carries a current of 1 A. Energy stored in the form of the magnetic field is [1]
 - a) 1 J
 - b) 0.1 J
 - c) 0.5 J
 - d) 0.05 J

- a) there is no wastage of power
b) choke is compact in size
c) choke is a good absorber of heat
d) choke is cheap
29. Relation between r.m.s. voltage and instantaneous voltage of an AC [1]
a) $V_0 = \frac{V_{\text{rms}}}{\sqrt{2}}$
b) $V_{\text{rms}} = 0.707 V_0$
c) Both $V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$ and $V_{\text{rms}} = 0.707 V_0$
d) $V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$
30. To reduce the resonant frequency in an LCR series circuit with a generator [1]
a) dielectric in the capacitor should be removed
b) the generator frequency should be reduced
c) another capacitor should be added in parallel to the first
d) the iron core of the inductor should be removed
31. The best material for the core of a transformer is: [1]
a) soft iron
b) mild steel
c) hard steel
d) stainless steel
32. The primary winding of a transformer has 50 turns and its secondary has 500 turns. If the primary is connected to a.c. supply of 20 V-50 Hz, then secondary will have an [1]
a) 200 V - 50 Hz
b) 2 V - 5 Hz
c) 200 V - 500 Hz
d) 2 V - 50 Hz
33. The primary winding of a transformer has 500 turns, whereas its secondary has 5,000 turns. The primary is connected to an a.c. supply 20 V-50 Hz. The secondary will have an output of: [1]
a) 200 V - 50 Hz
b) 200 V - 500 Hz
c) 2 V - 50 Hz
d) 2 V - 5 Hz
34. In an LRC series circuit $R = 300.0 \Omega$, $X_C = 300.0 \Omega$ and $X_L = 500.0 \Omega$. The average power consumed in the resistor is 60.0 W. Rms voltage of the source is [1]
a) 151 V
b) 141 V
c) 161 V
d) 131 V
35. A series circuit consists of an ac source of variable frequency, a 115.0Ω resistor, a $1.25 \mu\text{F}$ capacitor, and a 4.50-mH inductor. The impedance of this circuit when the angular frequency of the ac source is adjusted to half the resonant angular frequency is [1]
a) 156.0Ω
b) 166.0Ω
c) 176.0Ω
d) 146.0Ω
36. A 50 mH coil carries a current of 2A. The energy stored in the coil is: [1]
a) 0.1 J
b) 10 J
c) 0.5 J
d) 0.05 J
37. The selectivity of a series LCR a.c. circuit is large, when [1]
a) L is small and R is small
b) L is large and R is small

a) $R + X_L + X_C$

b) $\sqrt{\frac{1}{X_C^2} + \frac{1}{X_L^2} + R^2}$

c) $\sqrt{X_L^2 - X_C^2 + R^2}$

d) $\sqrt{R^2 + (X_L - X_C)^2}$

56. A transformer has 500 primary turns and 10 secondary turns. If the secondary has a resistive load of 15Ω , the currents in the primary and secondary respectively, are [1]

a) $3.2 \times 10^{-3} \text{ A}, 3.2 \times 10^{-3} \text{ A}$

b) $3.2 \times 10^{-3} \text{ A}, 0.16 \text{ A}$

c) $0.16 \text{ A}, 3.2 \times 10^{-3} \text{ A}$

d) $0.16 \text{ A}, 0.16 \text{ A}$

57. The primary and secondary coils of a transformer have 50 and 1500 turns respectively. If the magnetic flux ϕ linked with the primary coil is given by $\phi = \phi_0 + 4t$, where ϕ is in weber, t is time in second and ϕ_0 is a constant, the output voltage across the secondary coil is: [1]

a) 90 V

b) 220 V

c) 120 V

d) 30 V

58. In a series LCR circuit, the capacitance is changed from C to $\frac{C}{4}$. For the resonant frequency to remain unchanged, the inductance should be changed from L to nL, where n is: [1]

a) 2

b) $\frac{1}{2}$

c) 4

d) $\frac{1}{4}$

59. In a circuit, the current lags behind the voltage by a phase difference of $\pi/2$. The circuit contains which of the following? [1]

a) R and C

b) only C

c) only L

d) only R

60. An electric bulb marked 40 W and 200 V is used in a circuit of supply voltage 100 V. Its power would be: [1]

a) 20 W

b) 100 W

c) 10 W

d) 40 W

61. In a pure inductive circuit, the current [1]

a) lags behind the applied emf by an angle π

b) and applied emf are in same phase

c) lags behind the applied emf by an angle $\frac{\pi}{2}$

d) leads the applied emf by an angle $\frac{\pi}{2}$

62. Which quantity is increased in a step-down transformer? [1]

a) Current

b) Power

c) Frequency

d) Voltage

63. An ideal inductor is connected across an AC source of voltage. The current in the circuit [1]

a) lags voltage in phase by π .

b) lags voltage in phase by $\frac{\pi}{2}$.

c) is ahead of voltage in phase by $\frac{\pi}{2}$.

d) is ahead of the voltage in phase by π .

64. A transformer is used to light a 100 watt and 110 volt lamp from a 220 volt mains. If the main current is 0.5 ampere, the efficiency of the transformer is approximately [1]

a) 90%

b) 30%

c) 20%

d) 10%

4.50-mH inductor. Impedance of this circuit when the angular frequency of the ac source is adjusted to twice the resonant angular frequency is

a) 146 Ω

b) 176 Ω

c) 166 Ω

d) 156 Ω

75. Domestic power supply in India is

[1]

a) 110 V, 60 Hz

b) 220 V, 50 Hz

c) 416 V, 60 Hz

d) 24 V DC