

2024
UPDATED
SYLLABUS


PHYSICS

NCERT - 12



- ✓ Useful for CBSE, JEE & NEET exams
- ✓ Each topic contains Detailed Theory with images
- ✓ Every topic contains Exercises and Detailed solutions

3. CURRENT ELECTRICITY

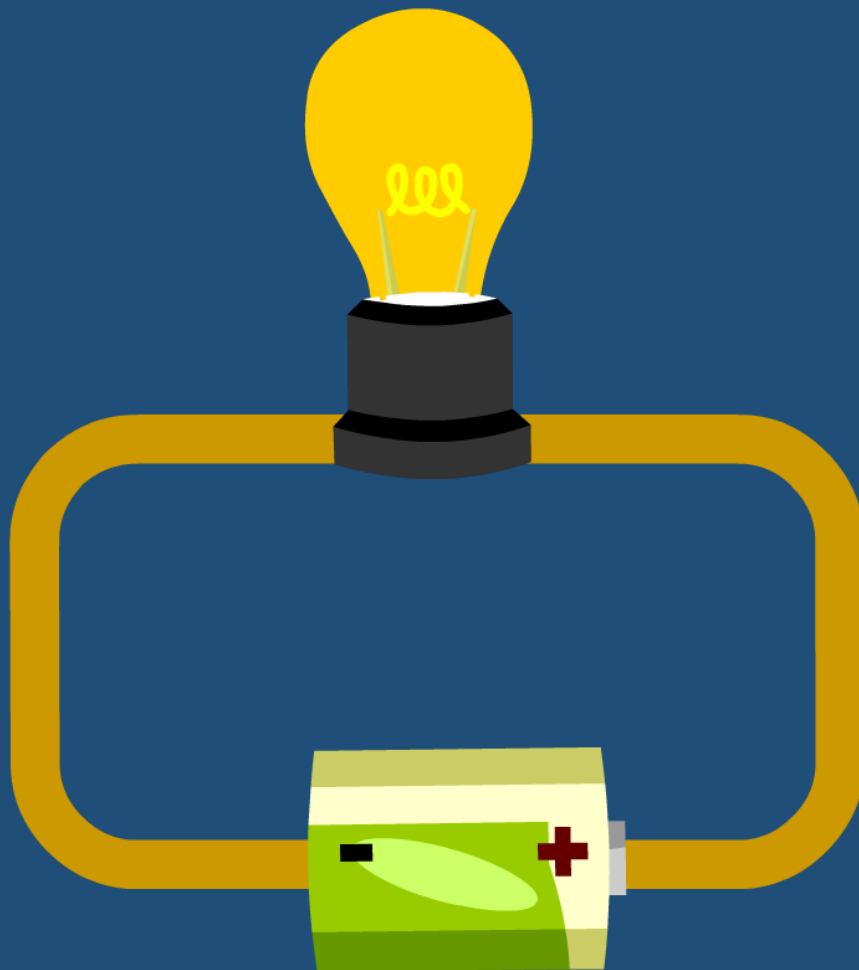

Physics Smart Booklet


**Theory + NCERT MCQs + Topic Wise
Practice MCQs + NEET PYQs**

Resistance depending on temperature

- Resistivity of conductor increase with increase in temperature.
- Resistivity of semiconductor decreases with increase in temperature

Ohm's Law

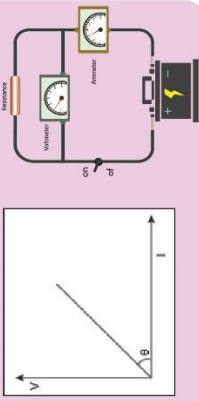- If physical condition remain same current $I \propto V \Rightarrow V = IR$
- R-electric resistance substances which obey Ohm's law called Ohmic and that do not obey called non-ohmic substances.
- Ohm's law is not valid for semi-conductor
- For Ohmic substances $\tan \theta = \frac{V}{I} = R$



Conductivity (σ) = $\frac{1}{\text{Resistivity } \rho}$

Unit = $\frac{1}{\Omega \cdot \text{m}}$ or $\frac{\text{mho}}{\text{ohm} \cdot \text{m}}$

Grouping of Resistance

Series grouping of resistance

- Equivalent resistance $R_0 = R_1 + R_2 + R_3 \dots$
- Current flow through each resistance is same.
- Potential difference, $V \propto R$

Some Important Formula

- After stretching, its length increases by N times then resistance will increase by N^2 times i.e.,

If radius be reduced to $\frac{1}{n}$ times then area of cross-section decreases n^2 time so the resistance become n^4 times i.e., $R_2 = n^4 R_1$

Using n conductors of equal resistance, the number of possible combination is $2^n - 1$.

If the resistance of n conductors are totally different, then the numbers of possible combination will be 2^n .

Electric Current

Rate of flow

S.I Unit Amperes (A) Coulomb Second

Instantaneous, $i = \frac{dq}{dt}$ Average, $i = \frac{\Delta q}{\Delta t}$

By convection, direction of flow of positive charge is taken as direction of flow of current. Drift velocity (V_d)

Drift velocity (V_d)

$i = neAv_d = neA \left(\frac{V}{\rho l n e A} \right) = \frac{V}{\rho l}$

Average uniform velocity acquired by free electron.

$V_d = \frac{j}{neA} = \frac{V}{\rho l n e A}$ or $\frac{eE}{m}$

$V_d = \mu_e E$ (μ_e is avg. time between collisions)

mobility, $\mu_e = \frac{V_d}{E}$ (ρ is resistivity unit is $\Omega \cdot \text{m}$)

In terms of relaxation time τ

$R = \frac{m l}{ne^2 A}$ and $\rho = \frac{m}{ne^2 \tau}$

n , τ , and ρ are properties of material.

Electric Energy and Power

Principle of bulb

- Resistance of bulb, $R = \frac{V^2}{P}$ or $R \propto \frac{1}{P}$ (V and P is rated value on bulb)
- In parallel, $P = P_1 + P_2$
- In Series, $\frac{1}{P} = \frac{1}{P_1} + \frac{1}{P_2}$
- In parallel a bulb having more rated power glows more brightly.
- In series a bulb having less rated power glows more brightly.

Heat energy developed across a resistor

$H = I^2 R t$, $t = \text{time}$

Power, $P = I^2 R = \frac{V^2}{R}$

For transmission cable, power loss, $\rho_s = I^2 R_c = \frac{P^2 R_c}{V_c^2}$, $P = \text{const.}$

Grouping of cells

Cell in series.

Current in the circuits, $I = \frac{Ne}{R + nR}$

Current in the circuit, $I = \frac{e}{R + \frac{r}{m}}$

Kirchoff's laws

1st Law/ Junction Law

- Algebraic sum of all the current meeting at junction is zero. i.e., $\sum i = 0$

2nd Law/ Loop rule

- Algebraic sum in potential around any closed loop is zero

Meter bridge Based on wheat stone bridge

$\frac{P}{Q} = \frac{R}{S} = \frac{l}{100-l} = S$

Balanced Condition of wheat stone bridge

$\frac{P}{Q} = \frac{R}{S}$


Potential gradient (x)

$x = \frac{V}{L} = \frac{\text{Volt}}{\text{m}}$


where, $V = IR = \left(\frac{E}{R + r_1 + r_2} \right) \times \frac{R}{L}$

Sensitivity of potentiometer

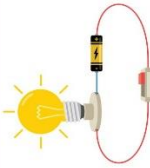- A potentiometer is more sensitive, if its potential difference measures a small potential difference more accurately.



Resistance colour code

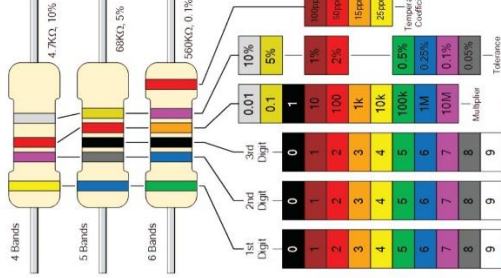

When cell is discharging

When cell is discharging current inside the cell is from cathode to anode current $I = \frac{E}{r + R}$

or $E = IR + Ir = V + Ir$ or $V = E - Ir$

When cell is charging

When cell is charging current inside the cell is from anode to cathode.

Current, $I = \frac{V - E}{r}$ or $V = E + Ir$

When cell is open circuit

$R = \infty$
 $I = \frac{E}{R + r} = 0$ and $V = E$

When cell is short circuited


$R = 0$ and $I = \frac{E}{r}$ and $V = IR = 0$

Power transferred to load by cell

$P = I^2 R = \frac{E^2 R}{(r + R)^2}$ and $P = P_{\text{max}}$

if $\frac{dP}{dR} = 0$ and $P = P_{\text{max}}$ if $r = R$

$P_{\text{max}} = \frac{E^2}{4r}$

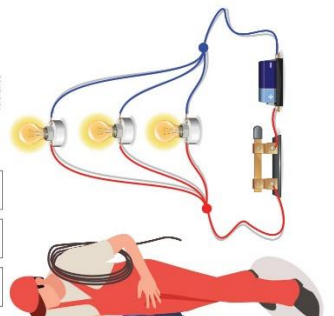

Current Electricity

Charges in motion constitute an **electric current**. A conductor offers a path for current. Application of potential difference across a conductor causes current. Potential difference can be provided using a cell or a battery (group of cells).

Current in a circuit in a single direction is called a direct current (dc), while a current whose direction keeps reversing at regular intervals and whose magnitude keeps changing continuously is called alternating current (ac).

Current carriers (mobile charge carriers): The charged particles whose drift in a definite direction constitutes the electric current are called current carriers.

Conventional current in a metallic conductor: In metallic conductors, negatively charged particles, namely electrons, drift under the influence of applied potential difference. This constitutes an **electron current**.

The direction of drift of positive charges is the direction of current. This current is called conventional current. The direction of conventional current is opposite to that of drift of electrons.

Strength of electric current: Electric current is the net flow of charge per second across a surface.

If ΔQ is the amount of charge that passes through an area in a time interval Δt , then the average current in the given time interval is, $I_{av} = \frac{\Delta Q}{\Delta t}$.

The instantaneous current is given by $I = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt}$

If the current is steady, then $I = \frac{Q}{t}$ where Q is the charge flowing across a section of a conductor in an interval of time t .

- The SI unit of current is ampere (A). 1 ampere = 1 coulomb per second.
- Since 1 coulomb = 6.25×10^{18} electrons, a flow of 6.25×10^{18} electrons per second is equal to 1 ampere of current.

Material	Mobile charge carriers
• Metallic conductors	Free electrons
• Liquid conductors	Positive ions and Negative ions
• Semiconductors	Free electrons and Holes
• Gaseous conductors	Positive ions and free electrons
• Super conductors	Cooper pairs (a pair of electrons with opposite spins)


Current density (\vec{j})

- If current i is uniformly distributed over an area S and is perpendicular to it, then

$$j = \frac{i}{S}$$

- Current density is a vector quantity. The direction of current density is the same as the direction of motion of positive charges.
- SI unit of current density is Am^{-2} .

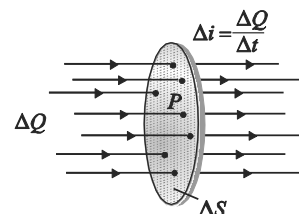- Relation between current and current density is $i = \int_S \vec{j} \cdot d\vec{S}$ over a finite area S .



Drift velocity of free electrons

- Drift velocity of **electrons** is given by $\vec{v}_d = -\frac{e\vec{E}}{m}\tau$ where $e \rightarrow$ charge on the electron, $m \rightarrow$ mass of the electron, $E \rightarrow$ electric field, $\tau \rightarrow$ relaxation time.
- The random speed of free electrons in a metallic conductor depends on the temperature and is of the order of 10^6 ms^{-1} . The drift speed of the free electrons is of the order of 10^{-4} ms^{-1} .

Relaxation time and mean free path: The average time elapsed between two successive collisions of a free electron with the metal ions in a conductor is called **relaxation time**, denoted by τ . The average distance traveled by an electron between two successive collisions is called the **mean free path**, denoted by λ .

Mobility (μ)

- The mobility (μ) of charge carriers is given by $\mu = v_d / E$ and its unit is $\text{m}^2\text{V}^{-1}\text{s}^{-1}$.
- The mobility of electrons and conductivity of a material are related by the expression $\sigma = ne\mu$ for a metallic conductor and $\sigma = n_e e \mu_e + n_h e \mu_h$ for a semiconductor where n_e is electron density, n_h is hole density, μ_e is electron mobility, μ_h is hole mobility.

Expression for current and current density in terms of drift speed

• $I = nAev_d$ and $\vec{J} = ne\vec{v}_d$

where n is the number of electrons per unit volume of a metallic conductor of cross sectional area A and e is the charge on the electron.

Ohm's law: Mathematically Ohm's law is expressed as $V = IR$

where, R is a constant of proportionality called resistance of the conductor.


- We have $R = \frac{V}{I}$. The SI unit of resistance is ohm (Ω). 1 ohm = 1 volt per ampere.
- The dimensional formula is $[\text{I}^{-2}\text{ML}^2\text{T}^{-3}]$.

At a given temperature, $R \propto \frac{l}{A}$ or $R = \rho \frac{l}{A}$ where $\rho =$ specific resistance or resistivity of the material of the conductor.

$R = \frac{m}{ne^2\tau} \times \frac{l}{A} = \frac{\rho l}{A}$ where ρ is the specific resistance of the material and

- For a conductor of length l having a circular cross-section, the resistance of the conductor is $R = \frac{\rho l}{\pi ab}$

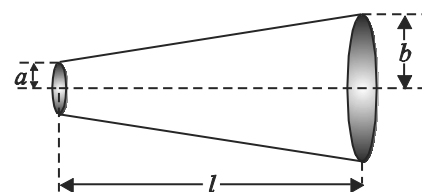(Here the radius of cross-section varies linearly from a to b and $(b - a) \ll l$).



Conductivity (σ)

- It is the reciprocal of resistivity. The SI unit of σ is siemen m^{-1}
- The dimensional formula for σ is $[\text{I}^2\text{M}^{-1}\text{L}^{-3}\text{T}^3]$.

Conductance (G)

- It is the reciprocal of resistance i.e. $G = \frac{1}{R} \Rightarrow G = \frac{A}{\rho l} = \frac{\sigma A}{l}$. The SI unit of G is siemen (S).
- The dimensional formula is $[\text{I}^2\text{M}^{-1}\text{L}^{-2}\text{T}^3]$.

Relation between J, σ and E (Ohm's law in vector form)


Current density, conductivity and electric field are related by $J = \sigma E$. In vector form, $\vec{J} = \sigma \vec{E}$.

Limitations of Ohm's Law

- Ohm's law is applicable only to metallic conductors at moderate temperatures and moderate potential differences.
- Ohm's law cannot be applied
 - to conductors maintained at very high temperatures or very low temperatures.
 - to semiconductors and semi conducting devices.
 - to conductors across which very high pd or very low pd is applied.

V-I characteristics

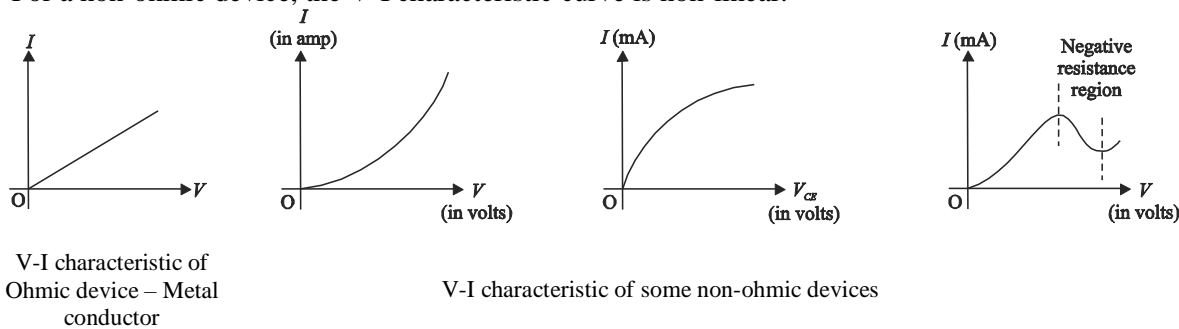- The variation of current (I) with voltage (V) at various temperatures for any device is called its V-I characteristics.
- For an ohmic device, V-I characteristic is linear.
- For a non-ohmic device, the V-I characteristic curve is non-linear.



Effect of temperature on resistance


- The resistivity ρ of a material depends on its temperature. For a small variation of temperature, $\rho = \rho_0(1 + \alpha(T - T_0))$, where α = temperature coefficient of resistance of the material.
- The resistance of a conductor at absolute temperature T is given by the relation $R_T = R_0(1 + \alpha(T - T_0))$

$$\alpha = \frac{(R_T - R_0)}{R_0(T - T_0)} = \frac{1}{R_0} \left(\frac{\Delta R}{\Delta T} \right)$$

- SI unit of α is $\frac{1}{\text{kelvin}}$ (K^{-1}).

- R versus t ($^{\circ}C$) graph; y-intercept $\rightarrow R_0$, slope = $R_0\alpha$
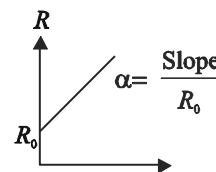
$$\Rightarrow \alpha = \frac{\text{slope}}{\text{y-intercept}}$$




- Alloys generally have a low temperature coefficient of resistance. In other words, their resistance values do not vary appreciably with change of temperature. It is for this reason that manganin and constantan coils are used in resistances boxes.
- Semiconductors have negative temperature coefficient of resistance while metals have positive temperature coefficient of resistance.

Thermistor

- Thermistors are made of semiconducting oxides of metals and hence it is a non-ohmic device.
- The resistance of a thermistor is given by $R = ae^{b/T}$ where a and b are constants for a material.

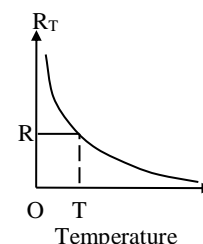- The temperature coefficient of resistance of material of a thermistor is given by $\alpha = -\frac{b}{T^2}$



- If R_1 and R_2 are resistances of a thermistor at two temperatures T_1 K and T_2 K respectively, then it can be shown that $\alpha = \frac{2.303(\log R_1 - \log R_2)}{(T_1 - T_2)}$.



Memory tip: B.B.ROY of Great Britain had a Very Good Wife.

The bold letters indicate the first letters of the colours in the sequence 0, 1, 2, 3, 4, 5, 6, 7, 8 and 9.


For resistors of value less than 10 ohm, the third band is either gold or silver such that the multiplying factor will be 0.1 or 0.01 respectively.

	Resistors in series	Resistors in parallel
1.	Current is same through all the resistors.	Voltage is same across each resistor.
2.	$V = V_1 + V_2 + V_3 + \dots$	$I = I_1 + I_2 + I_3 + \dots$
3.	$R_s = R_1 + R_2 + R_3 + \dots$	$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
4.	R_s is greater than the greatest of the individual resistances.	R_p is smaller than the smallest of the individual resistances.
5.	The applied voltage divides across the resistors according to the ratio $V_1 : V_2 : V_3 = R_1 : R_2 : R_3$ and hence the series combination is an voltage divider.	The current divides through the resistors in the ratio $I_1 : I_2 : I_3 = \frac{1}{R_1} : \frac{1}{R_2} : \frac{1}{R_3}$. Hence, the parallel combinations is called the current divider.
6.	If n identical resistors, each of resistance R are connected in series, then their effective resistance is $R_s = nR$.	For n identical resistors in series $R_s = nR$. Therefore $\frac{R_s}{R_p} = \frac{nR}{\left(\frac{R}{n}\right)} = n^2$ If n identical resistors, each of resistance R are connected in parallel, then their effective resistance is given by $\frac{1}{R_p} = \frac{n}{R} \therefore R_p = \frac{R}{n}$
7.	When a series combination of resistors is connected to a supply voltage, higher resistance dissipates more power, since $P = I^2R$; I is the common current through the resistors.	If there are two resistors R_1 and R_2 in parallel, then their effective resistance. $R_p = \frac{R_1 R_2}{R_1 + R_2}$ When a parallel combination of resistors is connected to a supply voltage, the lower resistance dissipates more power. $P = \frac{V^2}{R}$; V is common potential across the resistors.

Branch current

Current in one branch = $\frac{\text{main current} \times \text{resistance in the other branch}}{\text{sum of the resistances}}$
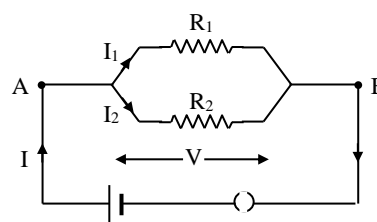
$$I = I_1 + I_2 \Rightarrow I_1 = \frac{IR_2}{R_1 + R_2} \text{ and } I_2 = \frac{IR_1}{R_1 + R_2}$$



Cell

- An energy source used to drive charges and hence establish electric current in a circuit.
- A combination of cells is called a **battery**.

Ohm's law applied to a closed circuit

- When the cell drives a current through a circuit, work has to be done to drive current through (1) the external resistance and (2) the internal resistance.

$$E = \text{pd across } R + \text{pd across } r = I(R + r)$$

- $I = \frac{E}{R + r}$

- Terminal pd across the cell, $V = IR = \frac{ER}{R + r}$. Also $V = E - Ir$

State of cell in a circuit	Terminal pd (V)	Current (I)	Resistance (R)
Open	$V = E$	$I = 0$	$R = \infty$
Closed	$V = E - Ir$ (During discharge) $V = E + Ir$ (During charging)	$I = \text{finite}$	$R = \text{finite}$
Short	$V = 0$	$I = \infty$	$R = 0$

Grouping of cells

Cells are grouped to get the necessary voltage and current.

Cells in series

For m identical cells in series, $E_{\text{eff}} = mE$

$$R_{\text{eff}} = R + mr = R + mr \text{ and } I = \frac{mE}{R + mr}$$

For m non-identical cells in series conjunction,


$$E_{\text{eff}} = E_1 + E_2 + \dots + E_m = \Sigma E_i$$

$$R_{\text{eff}} = R + (r_1 + \dots + r_m) = R + \Sigma r_i ; I = \frac{\Sigma E_i}{R + \Sigma r_i}$$

If p cells in a group of m identical cells are connected wrongly then

$$E_{\text{eff}} = (m - 2p)E$$
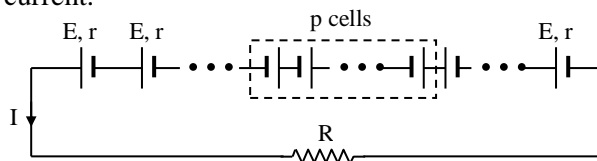
$$r_{\text{eff}} = mr ; I = \frac{(m - 2p)E}{R + mr}$$



Cells in parallel

1. For n identical cells in parallel, $E_{\text{eff}} = E$ and $r_{\text{eff}} = \frac{r}{n}$; $I = \frac{nE}{nR + r}$

2. For n non identical cells in parallel,

$$E_{\text{eff}} = \frac{\left(\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3} + \frac{E_4}{r_4} + \frac{E_5}{r_5} + \dots + \frac{E_n}{r_n} \right)}{\left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \frac{1}{r_4} + \dots + \frac{1}{r_n} \right)}, \quad r_{\text{eff}} = \frac{1}{\frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}}$$


3. In a parallel grouping of n non identical cells if some cells in parallel grouping are wrongly connected then

$$E_{\text{eff}} = \frac{\sum \frac{E_i}{r_i} - \sum \frac{E_j}{r_j}}{\sum \left(\frac{1}{r_i} + \frac{1}{r_j} \right)} = \frac{\left(\frac{E_1}{r_1} + \frac{E_2}{r_2} - \frac{E_3}{r_3} - \frac{E_4}{r_4} + \frac{E_5}{r_5} + \dots + \frac{E_n}{r_n} \right)}{\left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \frac{1}{r_4} + \dots + \frac{1}{r_n} \right)}$$

$$r_{\text{eff}} = \frac{1}{\frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}}$$

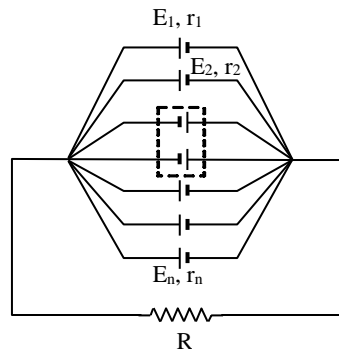Example: If any two cells are in parallel then

$$E_{\text{eff}} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2}}{\frac{1}{r_1} + \frac{1}{r_2}} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}, \quad r_{\text{eff}} = \frac{r_1 r_2}{r_1 + r_2}$$



Mixed grouping of cells

Let m identical cells each of emf E and internal resistance r be connected in series. Let n such rows of series cells be connected in parallel. Let the combination be connected across the resistance R.

- $I = \frac{mnE}{nR + mr}$
- The condition for maximum current in mixed grouping of cells is
External resistance = effective internal resistance $R = mr / n$
- Maximum current given by mixed grouping of cells, $I_{\text{max}} = \frac{mnE}{2\sqrt{mnrR}}$.



- When $R \gg r_{\text{eff}}$, series grouping is preferred.
- When $R \ll r_{\text{eff}}$, parallel grouping is preferred.
- To get more power, cells must be connected in mixed grouping.

Maximum power transfer theorem

Whenever internal resistance is equal to the external resistance, the power transferred by a cell is maximum. This is called maximum power transfer theorem.


$$P_{\text{max}} = I^2 R = \left(\frac{E}{R + r} \right)^2 R = \frac{E^2}{(2R)^2} R = \frac{E^2}{4R} \quad \text{or} \quad P_{\text{max}} = \frac{E^2}{4r}$$

Electrical energy and power

Heat dissipated in a conductor is $H = VI t = (V^2 / R)t = I^2 R t$ and $P = VI = (V^2 / R) = I^2 R$

Kirchhoff's Law

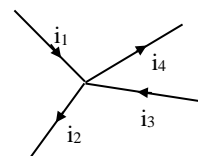- Kirchhoff's first law:** This law is also known as junction rule or current law (KCL). to this, the algebraic sum of currents meeting at a junction zero. In a circuit, at any junction the sum of the currents entering the junction must equal the sum of the currents leaving the junction $i_1 + i_3 = i_2 + i_4$.




According to this, the algebraic sum of currents meeting at a junction is zero, i.e., $\sum I = 0$. equal the

This law is simply a statement of "conservation of charge".


- Kirchhoff's second law:** This law is also known as loop rule or voltage law (KVL) and according to this, "the algebraic sum of the changes in potential in complete traversal of a mesh (closed loop) is zero", i.e., $\sum V = 0$.
- This law represents "conservation of energy"

- (ii) If there are n meshes in a circuit, the number of independent equations in accordance with loop rule will be $(n - 1)$.
- (3) **Sign convention for the application of Kirchhoff's law:** For the application of Kirchhoff's laws following sign convention is to be considered:

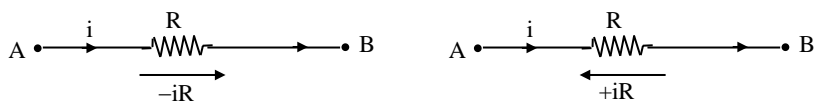- (i) The change in potential in traversing a resistance in the direction of current is $-iR$ while in the opposite direction is $+iR$.



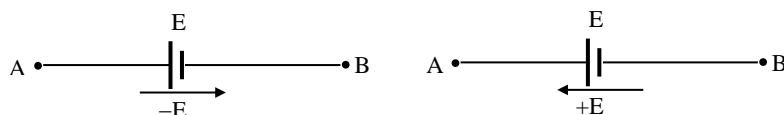- (ii) The change in potential in traversing an emf source from negative to positive terminal is $+E$ while in the opposite direction $-E$ irrespective of the direction on current in the circuit.



- (iii) The change in potential in traversing a capacitor from the negative terminal to the positive terminal is $+\frac{q}{C}$ while in opposite direction $-\frac{q}{C}$.

- (iv) The change in voltage in traversing an inductor in the direction of current is $-L\frac{di}{dt}$ while in opposite direction it is $+L\frac{di}{dt}$.

Measurement of resistance


The resistance of a wire can be determined using Wheatstone's network (bridge).

Principle of Wheatstone's bridge

Wheatstone's bridge consists of an arrangement of four resistances which can be used to measure one of the resistance in terms of the other resistances.

The bridge is said to be balanced when deflection in the galvanometer is zero. i.e., $i_g = 0$.

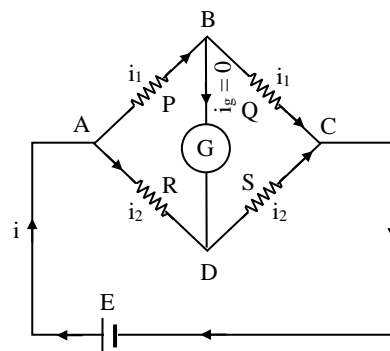This will happen when $\frac{P}{Q} = \frac{R}{S}$



- i. In Wheatstone bridge, cell and galvanometer arms are interchangeable.
- ii. If bridge is not balanced, current will flow from D to B if, $PS > RQ$

Potential gradient (x)


Potential difference (or fall in potential) per unit length of wire is called potential gradient i.e.,

$$x = \frac{V \text{ volt}}{L \text{ m}} \text{ where } V = iR = \left(\frac{e}{R + R_h + r} \right) \cdot R.$$

$$\text{So } x = \frac{V}{L} = \frac{iR}{L} = \frac{i\rho}{A} = \frac{e}{(R + R_h + r)} \cdot \frac{R}{L}$$


Application of Potentiometer

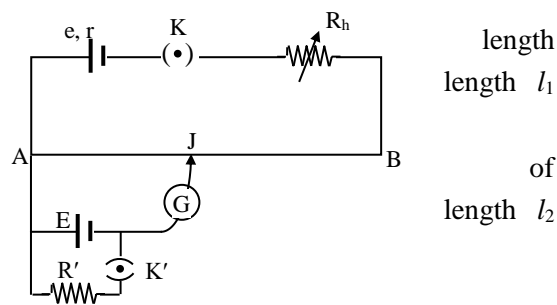- (1) To determine the internal resistance of a primary cell
- (i) Initially in secondary circuit key K' remains open and balancing (l_1) is obtained. Since cell E is in open circuit so its emf balances on i.e., $E = xl_1$
- (ii) Now key K' is closed so that cell E is in closed circuit. If the process balancing is repeated again then potential difference V balances on i.e., $V = xl_2$.
- (iii) By using formula internal resistance $r = \left(\frac{E}{V} - 1 \right) \cdot R'$



$$r = \left(\frac{l_1 - l_2}{l_2} \right) \cdot R'$$

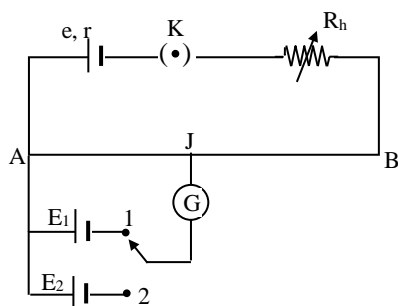- (2) **Comparison of emf's of two cells:** Let l_1 and l_2 be the balancing lengths with the cells E_1 and E_2 respectively, then $E_1 = xl_1$ and $E_2 = xl_2 \Rightarrow \frac{E_1}{E_2} = \frac{l_1}{l_2}$



Let $E_1 > E_2$ and both are connected in series. If balancing length is l_1 when cells assist each other and it is l_2 when they oppose each other as shown then:



$$(E_1 + E_2) = xl_1 \quad (E_1 - E_2) = xl_2$$

$$\Rightarrow \frac{E_1 + E_2}{E_1 - E_2} = \frac{l_1}{l_2} \quad \text{or} \quad \frac{E_1}{E_2} = \frac{l_1 + l_2}{l_1 - l_2}$$

Illustrations

1. In a current carrying metallic conductor, current density \vec{J} and drift velocity \vec{v}_d will be such that
 - (A) \vec{J} and \vec{v}_d will have opposite directions
 - (B) \vec{J} and \vec{v}_d will have the same direction
 - (C) the direction of \vec{J} is determined by the number of free electrons undergoing drift motion, where as the direction of \vec{v}_d remains same.
 - (D) the direction of \vec{v}_d is determined by the number of free electrons undergoing drift motion, where as the direction of \vec{J} remains same.

Ans (A)

$$\therefore R = \frac{H}{i^2 t} = \frac{400}{4 \cdot 10}$$

$$\therefore R = 10 \Omega$$

If current is doubled, then energy developed is,

$$H = (4)^2 \times (10) (10)$$

$$\therefore H = 1600 \text{ J}$$

\therefore Increase in the current by two times will increase the heat developed by 4 times

6. Two resistors are connected across a battery. Consider the following two statements.
 (a) The current through the circuit remains same and potential difference also remains same.
 (b) The current through each branch varies depending on the resistor used, where as voltage applied remains same.

Choose the correct option


- (A) a is true when 2 resistors are connected in series
 (B) b is true when 2 resistors are connected in parallel
 (C) both a and b are wrong
 (D) a is true when 2 resistors are connected in parallel

Ans (B)

Hint: When 2 resistors are connected in parallel current through each resistor varies and potential difference remains the same.

7. The potential difference between the points A and B is

- (A) 2 V (B) 20 V
 (C) -3 V (D) -20 V

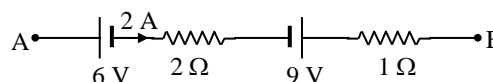

Ans (C)

Hint: $V_{AB} = -6 + (-2 \times 2) + 9 + (-2 \times 1) = -6 - 4 + 9 - 2 = -3 \text{ V}$

(Convention: Rise in potential is positive and fall in potential is negative)

8. In a metre bridge the balancing point is found to be at 39.5 cm from A, when the resistor Y = 12.5 Ω. The value of X is

- (A) 8.16 Ω (B) 1.68 Ω (C) 6.18 Ω (D) 12.5 Ω

Ans (A)


Hint: The balance condition for wheatstone's network is

$$\frac{X}{Y} = \frac{l_1}{100 - l_1}$$

$$\therefore X = \frac{l_1 Y}{100 - l_1} = \frac{39.5}{100 - 39.5} \times 12.5 \quad \therefore X = 8.16 \Omega$$

9. Figure shows a potentiometer circuit for comparison of 2 resistors. The balancing point with standard resistor R = 100 Ω is found to be 58.3 cm, while that of unknown resistance X is 68.5 cm. The value of X is

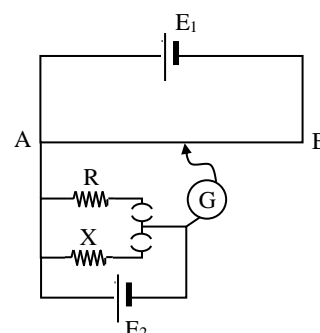- (A) 41.7 Ω
 (B) 11.75 Ω
 (C) 68.5 Ω
 (D) 100 Ω



Ans (B)

We know that

$$\frac{E_2}{E_1} = \frac{l_2}{l_1}$$

$$\text{Also } \frac{R_2}{R_1} = \frac{E_2}{E_1} = \frac{l_2}{l_1} \quad \therefore \frac{X}{R} = \frac{l_2}{l_1}$$

$$\therefore X = \left(\frac{l_1}{l_2} \right) R = \frac{68.5}{58.3} \times 10 \quad \therefore X = 11.75 \, \Omega$$

10. A galvanometer coil has a resistance $12 \, \Omega$ and the metre shows full scale deflection for a current of 3 mA . To convert the galvanometer into a voltmeter of range $0 - 18 \text{ V}$, we need to


- (A) Connect $5898 \, \Omega$ in series with the Galvanometer
- (B) Connect $5988 \, \Omega$ in series with the Galvanometer
- (C) Connect $5988 \, \Omega$ in parallel with the Galvanometer
- (D) Connect $5898 \, \Omega$ in parallel with the Galvanometer

Ans (B)
Hint: We know that, $V = I_g (R + G)$

$$\therefore R = \frac{V}{I_g} - G = \frac{18}{3 \times 10^{-3}} - 12 = 5988 \, \Omega$$

11. The potential at the points A and B in the following figure is

- (A) $V_A = V_B = 0$
- (B) $V_A = +E, V_B = -E$
- (C) $V_A = +E, V_B = +E$
- (D) none

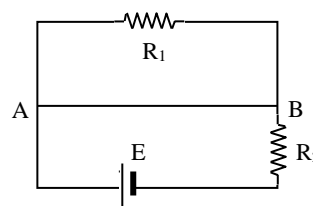
Ans (C)
Hint: A and B are at same potential, due to the fact that they have been connected by a common wire

This process is called as short circuiting

The potential difference across AB is zero.

12. A total of 6×10^{16} electrons pass through any cross-section of a conducting wire per second. The equivalent current is

Solution

$$i = \frac{ne}{t} = \frac{6 \times 10^{16} \times 1.6 \times 10^{-19}}{1} = 9.6 \text{ mA}$$

13. In a hydrogen atom, an electron moves in an orbit of radius $0.5 \, \text{\AA}$ with a speed of $2.2 \times 10^6 \text{ ms}^{-1}$. Calculate the equivalent current.

Solution

$$i = \frac{q}{t} = \frac{qV}{2\pi r} = \frac{1.6 \times 10^{-19} \times 2.2 \times 10^6}{2 \times \pi \times 5 \times 10^{-11}} = 1.12 \text{ mA}$$

14. The current through a wire depends on time as $i = i_0 + \alpha t$ where $i_0 = 10 \text{ A}$ and $\alpha = 4 \text{ As}^{-1}$. Find the charge that crosses through a section of wire in 10 second.

Solution

$$q = \int_{t_1}^{t_2} i \, dt = \int_0^{10} (i_0 + \alpha t) dt = \left[i_0 t + \alpha \frac{t^2}{2} \right]_0^{10}$$

$$\Rightarrow q = (10 \times 10) + \left[\frac{4 \times 100}{2} \right] = 300 \text{ C}$$

15. The area of cross section, length and density of a piece of metal of atomic mass 60 are 10^{-6} m^2 , 1.0 m and $5 \times 10^3 \text{ kg m}^{-3}$. Find the number of free electrons per unit volume and drift velocity when a current of 16 A pass through it. [Take $N = 6 \times 10^{23}$ and assume one free electron per atom]

Solution

$$\text{Mass of metal} = V \times d = 10^{-6} \times 1 \times 5 \times 10^3 = 5 \times 10^{-3} \text{ kg}$$

$$\therefore \text{Number of atoms in } 5 \text{ g of metal are } \frac{5 \times N}{60} = 5 \times 10^{22}$$

$$\text{Number of free electrons} = 5 \times 10^{22}$$

$$\text{Number of free electrons per unit volume} = 5 \times 10^{28} \text{ m}^{-3}$$

$$\therefore V_d = \frac{i}{neA} = \frac{16}{5 \times 10^{28} \times 1.6 \times 10^{-19} \times 10^{-6}} = 2 \times 10^{-3} \text{ ms}^{-1}$$

16. The amount of charge passing through cross section of wire is $q(t) = at^2 + bt + c$.

(i) write dimensions of a, b and c

(ii) If the values of a, b and c in S.I. units are 5, 3 and 1 respectively, find the value of current at $t = 5 \text{ s}$.

Solution

$$q = at^2 + bt + c$$

(i) According to principle of homogeneity, $[a] = \frac{q}{t^2} = [AT^{-1}]$

$$[b] = \frac{q}{t} = [A];$$

$$[c] = q = [AT]$$

(ii) Current $i = \frac{dq}{dt} = \frac{d}{dt}[at^2 + bt + c]$

$$\Rightarrow i = 10t + 3.$$

$$\text{At } t = 5 \text{ s, } i = 53 \text{ A}$$

17. A wire of resistance $4 \, \Omega$ is used to wind a coil of radius 7 cm. The wire has a diameter of 1.4 mm and the resistivity of wire is $2 \times 10^{-7} \, \Omega \text{ m}$. Find number of turns in coil.

Solution

If N be number of turns in coil then total length of wire is $l = 2\pi rN$

$$\text{Resistance } R = \frac{\rho l}{A} \Rightarrow l = \frac{RA}{\rho} = \frac{R\pi d^2}{4\rho}$$

$$\therefore 2\pi rN = \frac{R\pi d^2}{4\rho} \Rightarrow N = \frac{R\pi d^2}{4\rho \cdot 2\pi r}$$

$$\Rightarrow N = \frac{Rd^2}{8\rho r} = \frac{4 \times 1.96 \times 10^{-6}}{8 \times 2 \times 10^{-7} \times 7 \times 10^{-2}} = \frac{1.96 \times 10^3}{28}$$

$$\Rightarrow N = 70$$


18. A rectangular block has dimensions $5 \text{ cm} \times 5 \text{ cm} \times 10 \text{ cm}$ if its resistivity is $3.5 \times 10^{-5} \Omega \text{ m}$, calculate the resistance between two square ends and between two rectangular ends.

Solution

$$R_{12} = \frac{\rho l}{A} = \frac{3.5 \times 10^{-5} \times 10^{-1}}{25 \times 10^{-4}}$$

$$R_{12} = 1.4 \times 10^{-3} \Omega$$

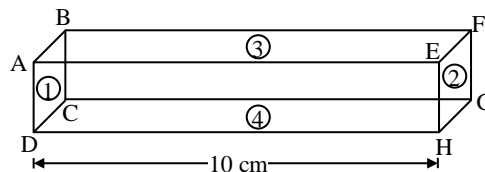
$$R_{34} = \frac{\rho l}{A'} = \frac{3.5 \times 10^{-5} \times 5 \times 10^{-2}}{50 \times 10^{-4}} = 3.5 \times 10^{-4} \Omega$$



Each of the following questions consists of a statement-I and a Statement-II. Examine both of them and select one of the options using the following codes

- (A) Statement-I and Statement-II are true and Statement-II is the correct explanation of Statement-I.
 (B) Statement-I and Statement-II are true, but Statement-II is not the correct explanation of Statement - I
 (C) Statement-I is true, but Statement -II is false
 (D) Statement-I is false, but Statement -II is true

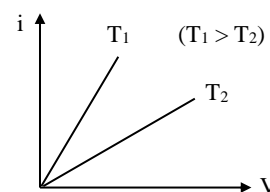19. **Statement-I:** i-V graph for a conductor at two different temperatures T_1 and T_2 is as shown. Then $T_2 > T_1$



Statement-II: Resistance of a conductor increases with rise in temperature.

Ans (A)

$$\text{We know } R = \frac{V}{I} = \frac{1}{\text{slope}}$$

$$\therefore R_2 > R_1. \text{ Hence } T_2 > T_1$$

20. **Statement-I:** A resistance wire is broken into 4 pieces and all are connected in parallel. The net resistance becomes $\frac{1}{16}$ times the earlier value.

Statement-II: In parallel net resistance is less than the smallest value of individual resistance.

Ans (B)

$$\frac{1}{R_{\text{eff}}} = \frac{4}{R} + \frac{4}{R} + \frac{4}{R} + \frac{4}{R} \quad \therefore R_{\text{eff}} = \frac{R}{16}$$

21. **Statement-I:** Potential difference across the terminals of a battery is always less than emf of the battery.

Statement-II: During discharging of a battery potential difference across the terminals of a battery is less than its emf.

Ans (D)

Hint: During charging of a battery $V = E + iR$

$$\therefore V > E$$

22. **Statement-I:** Two identical bulbs when connected in parallel across a battery consume a total power 'P'. When they are connected across the same in series total power consumed is $\frac{P}{4}$.

Statement-II: In parallel $P = P_1 + P_2$ and in series $P = \frac{P_1 P_2}{P_1 + P_2}$

Ans (A)

23. **Statement-I:** Resistance of an ammeter is less than the resistance of a milli ammeter

Statement-II: Value of shunt required in case of ammeter is more than a milli ammeter.

Ans (C)

In case of ammeter more current should pass through the shunt. Thus shunt resistance should be less or overall resistance of ammeter should be less.

24. **Statement-I:** kVA is the unit of electrical power and kWh is the unit of electrical energy.

Statement-II: Both kVA and kWh have same dimensions

Ans (C)

kVA is unit of power and kWh is unit of energy

25. **Statement-I:** If by mistake a voltmeter is connected in series it gets burnt

Statement-II: Current will drastically decrease in the circuit.

Ans (D)

Resistance of voltmeter is high. If it is connected in series then current will decrease but it will not be burnt.

26. **Statement-I:** Net power supplied by a non-ideal battery is $Ei - i^2r$

Statement-II: Power consumed by internal resistance of a battery is i^2r .

Ans (A)

27. **Statement-I:** For metallic conductors $\frac{V}{I} = R$, a constant.

Statement-II: V – I graph is always straight line passing through origin, for metallic conductors

Ans (A)

28. **Statement-I:** In our houses when we start switching on different light buttons, main current goes on increasing.

Statement-II: Different connections in houses are in parallel. When we start switching on different light buttons, net resistance of the circuit decreases. Therefore main current increases.

Ans (A)

Hint: In our houses, all intermediate connections are parallel connections, thus both are true and statement-II is the cause of statement-I.


29. **Statement-I:** Current between two points in an electrical circuit always flows from higher potential to lower potential.

Statement-II: During discharging of a battery current inside the battery flows from higher potential to lower potential.

Ans (C)


Current through a resistance wire flows from higher potential to power potential.

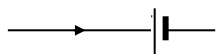During charging of a battery current flows from [+ to negative] as shown in the figure.



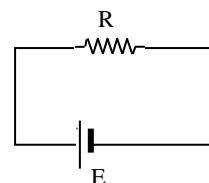30. **Statement-I:** In the circuit shown in the figure, battery is ideal. If a resistance R_0 is connected in parallel with R. Power across R will decrease

Statement-II: Current drawn from the battery will increase.



Ans (D)

In both the cases potential difference across R is E

$$\therefore P = \frac{E^2}{R}$$

In second case, net resistance will decrease

\therefore Main current will increase

NCERT LINE BY LINE QUESTIONS

1. Estimate the average drift speed of conduction electrons in a conductor of cross-sectional area 10^{-7} m^2 carrying current of 1.5 A. The number density of conduction electrons is $8.5 \times 10^{28} \text{ m}^{-3}$.


(a) 2.2 mm s^{-1}

(b) 1.1 mms^{-1}

(c) 3.3 mm s^{-1}


(c) 0.1 mm s^{-1}

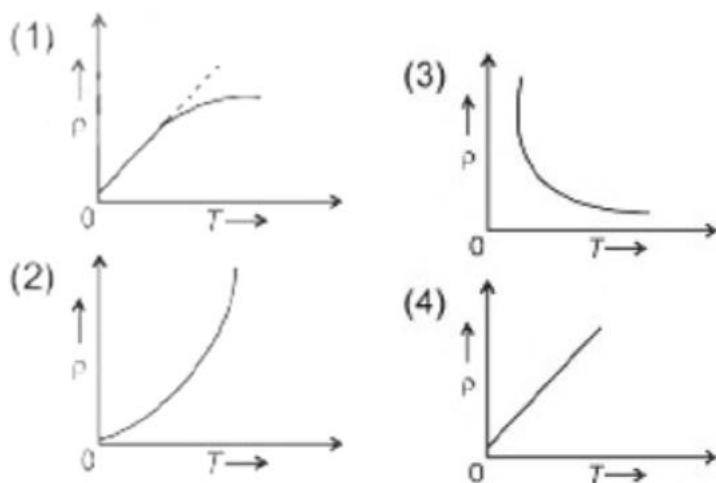2. Average collision time for electrons in a conductor under a certain potential difference is found to be 10^{-15} s. The mobility of electron in metal conductor is
- (a) $1.5 \times 10^{-3} \text{ m}^2/\text{Vs}$ (b) $2.2 \times 10^{-3} \text{ m}^2/\text{Vs}$
 (c) $2.9 \times 10^{-3} \text{ m}^2/\text{Vs}$ (c) $1.75 \times 10^{-4} \text{ m}^2/\text{Vs}$
3. A charged particle is having drift velocity of $7.5 \times 10^{-4} \text{ m s}^{-1}$ in an electric field of $3 \times 10^{-9} \text{ V m}^{-1}$. The electron mobility is
- (a) $2.5 \times 10^4 \text{ m}^2 \text{V}^{-1} \text{s}^{-1}$ (b) $2.5 \times 10^5 \text{ m}^2 \text{V}^{-1} \text{s}^{-1}$
 (c) $2.25 \times 10^{-13} \text{ m}^2 \text{V}^{-1} \text{s}^{-1}$ (c) $4.1 \times 10^3 \text{ m}^2 \text{V}^{-1} \text{s}^{-1}$
4. Arrange following materials in correct order of their conductivity. Nichrome, Copper, Germanium, Silver.
- (a) Silicon > Germanium > Nichrome > Copper
 (b) Silver > Copper > Germanium > Nichrome
 (c) Silver > Copper > Nichrome > Germanium
 (c) Germanium > Nichrome > Copper > Silver
5. The resistivity of alloy manganin
- (a) Increases rapidly with increase of temperature
 (b) Decreases linearly with increase in temperature
 (c) Increases rapidly with decrease in temperature
 (c) Is nearly independent of temperature
6. The graph of resistivity versus temperature for copper is best represented by graph shown below. The correct graph is




7. A resistor is marked with rings coloured as brown, black, green and gold. The resistance in ohm is
- (a) $(3 \times 10^6 \pm 5\%) \Omega$ (b) $(1.10 \times 10^5 \pm 5\%) \Omega$
 (c) $(10^6 \pm 5\%) \Omega$ (c) $(8.5 \times 10^6 \pm 5\%) \Omega$
8. Which among the following statements is correct?
- (a) In a metal, number density is independent of temperature
 (b) With increase in temperature, relaxation time in metal decreases
 (c) For semiconductors and insulators number density increases with increase in temperature
 (c) All the above

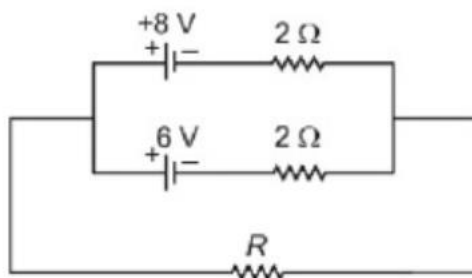9. Nichrome has resistance of 75.3Ω at 30°C . The resistance of nichrome becomes 85.8Ω when current passes through it, if average temperature coefficient of resistance of nichrome is $1.7 \times 10^{-4} \text{C}^{-1}$. The temperature of nichrome now is
 (a) 700°C (b) 750°C (c) 850°C (d) 900°C
10. The incorrect statement among the following statements is
 (a) Emf of a cell is the potential difference between its positive and negative electrodes in an open circuit
 (b) Internal resistance of dry cells is much higher than common electrolyte cells.
 (c) The terminal potential difference of a cell can be zero
 (d) When current passes from positive to negative terminal of a cell inside it, terminal potential difference is less than its emf.
11. When a current of 2 A flows in a battery from its negative to positive terminal, the potential difference across it is 12 V . If a current of 3 A is flowing in opposite direction it produces a potential difference of 15 V . The emf of the battery is
 (a) 12.6 V (b) 13.5 V (c) 14.0 V (d) 13.2 V
12. In the combination of two cells in parallel by joining positive terminals together and similarly two negative ones, the value of $\frac{E_{\text{eq}}}{r_{\text{eq}}}$ in circuit is




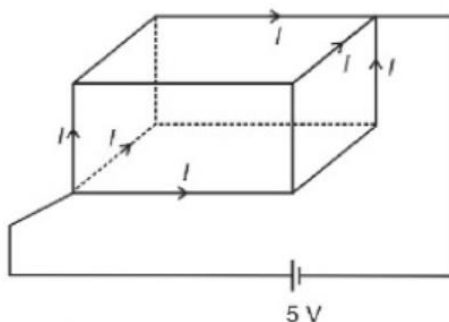- 1) 7 A (2) 10 A (3) 2 A (4) 8 A
13. When a metal conductor connected to right gap of meter bridge is heated, the balancing point from left end
 (a) Shifts towards left (b) Shifts towards right
 (c) Remains unchanged (d) Shift to zero position
14. Resistance P , Q , S and R are arranged in clockwise cyclic order to form a balanced wheatstone bridge. The ratio of electric power consumed in the branches ($P + Q$) and ($R + S$) is,
 1) $1 : 1$ (2) $R : P$ (3) $R^2 : P^2$ (4) $Q : S$
15. A battery of e.m.f. 5 V and negligible internal resistance is connected across the diagonally opposite corners of a cubical network consisting of 12 resistors of network each of resistance 1Ω . The current along one edge of the cube is




- 1) 1A 2) 2A 3) 3A 4) 4A

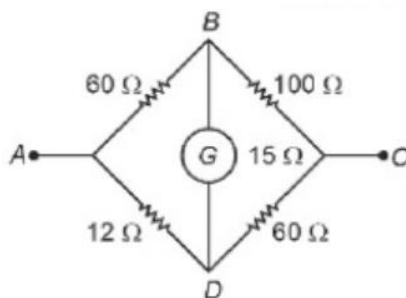16. Four arms of wheat-stone bridge have the following resistances. AB - 60Ω , BC = 100Ω , CD = 60Ω , DA = 12Ω . A galvanometer of 15Ω is connected across BD. Calculate the value of additional resistance connected across CD to balance the bridge.



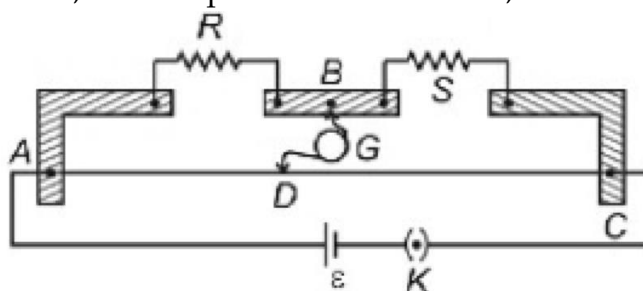- (a) 12Ω (b) 15Ω (c) 18Ω (d) 30Ω
17. In a Meter Bridge null point is found to be at 30 cm from end A. If now a resistance of 10Ω is connected in parallel with S, the null point occurs at 65 cm, value of S is nearly



- (a) 20Ω (b) 28Ω (c) 33Ω (d) 38Ω
18. In a potentiometer of 8 wires, the balance point is obtained on fifth wire. To Shift balance point to 6th wire, we should

- (a) Decrease resistance in main circuit
 (b) Increase resistance in main driver circuit
 (c) Decrease resistance in series with cell whose emf is to measure
 (d) Taking driver battery with higher emf
19. A potentiometer with driver battery of emf 2 V is used for determination of internal resistance of 1.5 V cell. The balance point of the cell in open circuit is 225 cm. When a resistance of 7.0Ω is used in external circuit across of the cell, the balance point shifts to 210 cm length of potentiometer wire. The internal resistance of the cell is

- (a) 1Ω (b) 0.5Ω (c) 2Ω (d) 5Ω
20. Pick out wrong statement about the Kirchhoff's laws of electric circuit.

- (a) Outgoing currents adds up and are equal to incoming currents at a junction
 (b) Electric potential in electric circuit is position dependent. Starting with any point if we come back to same point, total potential change must be zero
 (c) Junction rule is based on conservation of energy law
 (d) Bending or reorienting the wire does not change the validity of Kirchhoff's junction rule.

21. The rate of flow of an electric charge is known as :

- (a) electric potential (b) electric conductance
 (c) electric current (d) none of these

22. The SI unit of electric current is :

- (a) ohm (b) ampere (c) volt (d) faraday

23. The instrument used for measuring electric current is :
 (a)ammeter (b)galvanometer (c)voltmeter (d)potentiometer
24. The amount of work done in joules, when one unit electric charge moves from one point to another point in an electric circuit is called :
 (a)electric current (b)electric resistance
 (c)electric conductance (d)potential difference
25. The unit of potential difference is :
 (a)volt (b)ohm (c)ampere (d)faraday
26. The relation between potential difference (V) and current (I) is :
 (a) $V \propto I^2$ (b) $V \propto 1/I$ (c) $V^2 \propto I$ (d) $V \propto I$
27. The relation between potential difference (V) and current (I) was discovered by :
 (a)Newton (b) Ampere (c) Ohm (d) Volta
28. The obstruction offered by material of conductor to the passage of electric current is known as :
 (a)Resistance (b) Conductance (c) Inductance (d) None of these
29. The SI unit of resistance is :
 (a) Newton (b) Ohm (c) Watt (d) Joule
30. The resistance of a conductor is directly proportional to :
 (a) its area of cross-section (b) density
 (c) melting point (d) length
31. The resistance of a conductor is inversely proportional to its :
 (a) area of cross-section (b) length
 (c) specific heat capacity (d) density
32. A current of 2A flows through a conductor whose ends are at a p.d of 4V. The resistance of the conductor is :
 (a) 8 Ω (b) 0.5 Ω (c) 6 Ω (d) 2 Ω
33. The rheostat is used in the circuit to :
 (a) increase the magnitude of current only
 (b) decrease the magnitude of current only
 (c) increase or decrease the magnitude of current
 (d) none of these
34. During the verification of Ohm's law :
 (a) ammeter and voltmeter should be connected in series
 (b) ammeter should be connected in series and voltmeter in parallel
 (c)ammeter should be connected in parallel and voltmeter in series
 (d) ammeter and voltmeter should be connected in parallel
35. Which of the following laboratory apparatus is not used during the verification of Ohm's law :
 (a) Voltmeter (b) Ammeter (c) Galvanometer (d)Rheostat
36. A voltmeter is used to find p.d. in any electrical circuit which of the statement given below is true
 (a) A voltmeter is a high resistance instrument and is connected in series circuit
 (b) A voltmeter is a low resistance instrument and is connected in series circuit
 (c) A voltmeter is a high resistance instrument and is connected in parallel circuit
 (d)A voltmeter is a low resistance instrument and is connected in series circuit
37. Which of the following statement is not true, regarding the electrical set-up for the verification of Ohm's law:

- (a) The voltmeter is connected in parallel with the known resistance
 (b) The ammeter is connected in series circuit
 (c) The rheostat can only increase the resistance in electric circuit
 (d) The single key is used to switch on/off the electric circuit
38. When a 20V battery is connected across an unknown resistor there is a current of 50 mA in the circuit. Find the value of the resistance of the resistor:
 (a) $2500\ \Omega$ (b) $400\ \Omega$ (c) $0.4\ \Omega$ (d) none of these
39. A battery of 12V is connected in series with resistors of 0.2 ohm , 0.3 ohm, 0.4 ohm, 0.5 ohm and 12 ohm. How much current would flow through the 0.3 ohm resistor:
 (a) 0.895A (b) 1.11A (c) 0.5A (d) none of these
40. Among which of the following resistance does not depend :
 (a) length of conductor (b) area of cross-section
 (c) temperature (d) density
41. Electricity constituted by electric charges at rest on the surface of a conductor is called
 (a) Electricity (b) Potential difference
 (c) Current electricity (d) Static electricity
42. The closed path between two points at different potentials, to make the electric current flow is called
 (a) Electric circuit (b) Electric current (c) Electric potential (d) Electric cell.
43. Direction of conventional current is taken from
 (a) Negative to positive (b) Positive to negative
 (c) It could be from positive to negative or negative to positive
 (d) None of these.
44. With increase in temperature, resistance of a conductor
 (a) Decreases (b) Increases
 (c) May decrease or increase depending on temperature
 (d) It does not depend on temperature.
45. In series combination, resistance increases due to increase in
 (a) Temperature (b) Humidity (c) Length (d) Area of cross-section.
46. In parallel combination, resistance decreases due to increase in
 (a) Temperature (b) Humidity (c) Area of cross-section (d) Length.
47. The rate at which electricity is dissipated or consumed by an appliance is called electrical
 (a) current (b) Power (c) Potential (d) Energy.
48. The unit of electrical power is
 (a) watt (b) ampere (c) joule (d) ohm.
49. In series combination of electrical appliances, total electrical power
 (a) Increases (b) Decreases
 (c) May increase or decrease (d) Does not change.
50. In parallel combination of electrical appliances, total electrical power
 (a) Increases (b) Decreases
 (c) Does not change (d) Remain same.
51. The total work done by an electrical appliance during its operation, is called electrical
 (a) Current (b) Power (c) Energy (d) Potential
52. The number of joules in 1kWh is

67. The condition required to measure electric charge is:
 (a) Electric circuit (b) Electric current (c) Potential difference (d) Cell
68. A neutral body has:
 (a) Both types of positive and negative charges (b) Only positive charge
 (c) Only negative charge (d) No charge at all
69. Work done in moving a unit positive test charge from infinity to a point inside an electric field, is called:
 (a) Potential (b) Field (c) Field intensity (d) Potential difference
70. Work done in moving a unit positive test charge from one point to other inside an electric field, is called:
 (a) Potential (b) Field
 (c) Field intensity (d) Potential difference
71. How does resistance depend upon the length of a conductor?
 (a) The resistance is directly proportional to the length of a conductor
 (b) The resistance is inversely proportional to the length of a conductor
 (c) Both of the above (d) None of the above
72. What is the unit of resistivity?
 (a) Ohm-metre (b) Ohm-cm (c) Ohm-km (d) None of the above
73. Why is a metric bridge so called?
 (a) Since the bridge uses one metre long wire
 (b) Since the bridge contains many metre wire
 (c) Since the old name of the metre bridge is metre bridge
 (d) None of the above
74. Why the metric bridge is suitable for measuring moderate resistances?
 (a) The bridge is more sensitive for moderate values
 (b) The bridge is not sensitive for moderate values
 (c) The bridge is less sensitive for moderate values
 (d) None of the above
75. Why should current be passed for a short time?
 (a) Continuous current will increase the cost of consumption
 (b) Continuous current will cause unnecessary heating effecting values of resistances used
 (c) Both of the above (d) None of the above
76. In series combination of electrical appliances, total electric power:
 (a) Increases (b) Decreases
 (c) May increase or decrease according to the situation
 (d) No definite observation
77. The rate of work done or electric energy developed or consumed by a generator or appliance is called electric:
 (a) Current (b) Power (c) Potential (d) Energy
78. Heating of current carrying conductor is due to:
 (a) Loss of kinetic energy of moving atoms
 (b) Loss of kinetic energy of moving electrons
 (c) Attraction between electrons and atoms
 (d) Repulsion between electrons and atoms
79. In parallel combination, total resistance:
 (a) Decreases (b) Increases

- (c) May decrease or increase according to the situation
 (d) No particular observation
80. The decrease of resistance in parallel combination is due to:
 (a) The effective area of the cross-section decreases
 (b) The effective area of the cross-section increases
 (c) The effective area of the cross-section sometime increases, sometime decreases
 (d) None of the above
81. In parallel combination of electrical appliances, total electric power:
 (a) Increases (b) Decreases
 (c) May increase or decrease according to the situation
 (d) No definite observation
82. The electric appliances are connected in domestic line (Houseline):
 (a) In series (b) In parallel
 (c) Sometimes series, sometimes parallel (d) None of the above
83. Voltmeter is always connected with circuit in:
 (a) Serie (b) Parallel
 (c) Sometimes series sometimes parallel (d) None of the above
84. In which combination, Ammeter is connected with circuit:
 (a) Series (b) Parallel
 (c) Sometime series, sometimes parallel (d) None of the above

TOPIC WISE PRACTICE QUESTIONS


Topic 1: Electric Current, Drift of Electrons and Ohm's Law

- A flow of 106 electrons per second in a conducting wire constitutes a flow of current of
 (1) $1.6 \times 10^{-15} \text{ A}$ (2) $1.6 \times 10^{-11} \text{ A}$ (3) $1.6 \times 10^{-12} \text{ A}$ (4) $1.6 \times 10^{-13} \text{ A}$
- Relation between drift velocity (v_d) of electron and thermal velocity (v_t) of electron at room temp is expressed as
 (1) $v_d = v_t$ (2) $v_d > v_t$ (3) $v_d < v_t$ (4) $v_d = v_t = 0$
- For which of the following dependence of drift velocity v_d on electric field E , is Ohm's law obeyed?
 (1) $v_d \propto E^2$ (2) $v_d = E^{1/2}$ (3) $v_d = \text{constant}$ (4) $v_d = E$
- A current of 1 mA flows through a copper wire. How many electrons will pass through a given point in each second
 (1) 6.25×10^8 (2) 6.25×10^{31} (3) 6.25×10^{15} (4) 6.25×10^{19}
- A conducting wire of cross-sectional area 1 cm^2 has 3×10^{23} charge carriers per m^3 . If wire carries a current of 24 mA, then drift velocity of carriers is
 (1) $5 \times 10^{-2} \text{ m/s}$ (2) 0.5 m/s (3) $5 \times 10^{-3} \text{ m/s}$ (4) $5 \times 10^{-6} \text{ m/s}$
- At room temperature, copper has free electron density of 8.4×10^{28} per m^3 . The copper conductor has a cross-section of 10^{-6} m^2 and carries a current of 5.4 A. The electron drift velocity in copper is
 (1) 400 m/s (2) 0.4 m/s (3) 0.4 mm/s (4) 72 m/s
- The number of free electrons per 100 mm of ordinary copper wire is 2×10^{21} . Average drift speed of electrons is 0.25 mm/s. The current flowing is
 (1) 5 A (2) 80 A (3) 8 A (4) 0.8 A
- Two wires A and B of the same material, having radii in the ratio 1: 2 and carry currents in the ratio 4: 1. The ratio of drift speed of electrons in A and B is
 (1) 16: 1 (2) 1: 16 (3) 1: 4 (4) 4: 1

9. An Aluminium (Al) rod with area of cross-section $4 \times 10^{-6} \text{ m}^2$ has a current of 5 ampere. Flowing through it. Find the drift velocity of electron in the rod. Density of Al = $2.7 \times 10^3 \text{ kg/m}^3$ and Atomic wt. = 27. Assume that each Al atom provides one electron
 (1) $8.6 \times 10^{-4} \text{ m/s}$ (2) $1.29 \times 10^{-4} \text{ m/s}$ (3) $2.8 \times 10^{-2} \text{ m/s}$ (4) $3.8 \times 10^{-3} \text{ m/s}$
10. The belt of an electrostatic generator is 50 cm wide and travels at 30 cm/sec. The belt carries charge into the sphere at a rate corresponding to 10–4 ampere. What is the surface density of charge on the belt.
 (1) $6.7 \times 10^{-5} \text{ Cm}^{-2} / \text{s}$ (2) $6.7 \times 10^{-4} \text{ Cm}^{-2} / \text{s}$ (3) $6.7 \times 10^{-7} \text{ Cm}^{-2} / \text{s}$ (4) $6.7 \times 10^{-8} \text{ Cm}^{-2} / \text{s}$
11. In a neon gas discharge tube Ne^+ ions moving through a cross-section of the tube each second to the right is 2.9×10^{18} , while 1.2×10^{18} electrons move towards left in the same time; the electronic charge being $1.6 \times 10^{-19} \text{ C}$, the net electric current is
 (1) 0.27 A to the right (2) 0.66 A to the right (3) 0.66 A to the left (4) zero
12. A conductor carries a current of $50 \mu \text{ A}$. If the area of cross section of the conductor is 50 mm^2 , then value of the current density in Am^{-2} is
 (1) 0.5 (2) 1 (3) 10^{-3} (4) 10^{-6}
13. When the current i is flowing through a conductor, the drift velocity is v . If $2i$ current flows through the same metal but having double the area of cross-section, then the drift velocity will be
 (1) $v \sqrt{4}$ (2) $v / 2$ (3) v (4) $4v$


Topic 2: Resistance, Conductance and Resistivity

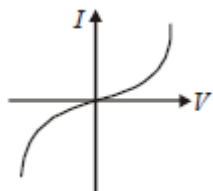14. The electric resistance of a certain wire of iron is R . If its length and radius are both doubled, then
 (1) the resistance and the specific resistance, will both remain unchanged
 (2) the resistance will be doubled and the specific resistance will be halved
 (3) the resistance will be halved and the specific resistance will remain unchanged
 (4) the resistance will be halved and the specific resistance will be doubled
15. If N , e , τ and m are representing electron density, charge, relaxation time and mass of an electron respectively, then the resistance of wire of length ℓ and cross-sectional area A is given by
 (1) $\frac{m\ell}{Ne^2A^2\tau}$ (2) $\frac{2m\tau A}{Ne^2\ell}$ (3) $\frac{Ne^2\tau A}{2m\ell}$ (4) $\frac{Ne^2A}{2m\tau\ell}$
16. The I - V characteristics shown in figure represents



- (1) ohmic conductors
 (2) non-ohmic conductors
 (3) insulators
 (4) superconductors
17. If a negligibly small current is passed through a wire of length 15 m and of resistance 5Ω having uniform cross section of $6 \times 10^{-7} \text{ m}^2$, then coefficient of resistivity of material, is
 (1) $1 \times 10^{-7} \Omega\text{-m}$ (2) $2 \times 10^{-7} \Omega\text{-m}$ (3) $3 \times 10^{-7} \Omega\text{-m}$ (4) $4 \times 10^{-7} \Omega\text{-m}$
18. Two copper wires have their masses in the ratio 2 : 3 and the lengths in the ratio 3 : 4. The ratio of their resistances is
 (1) 4 : 9 (2) 27 : 32 (3) 16 : 9 (4) 27 : 128
19. The masses of the three wires of copper are in the ratio of 1 : 3 : 5 and their lengths are in the ratio of 5 : 3 : 1. The ratio of their electrical resistance is
 (1) 1 : 3 : 5 (2) 5 : 3 : 1 (3) 1 : 25 : 125 (4) 125 : 15 : 1
20. A certain piece of copper is to be shaped into a conductor of minimum resistance. Its length and diameter should be respectively
 (1) ℓ , d (2) 2ℓ , d (3) $\ell/2$, $2d$ (4) 2ℓ , $d/2$
21. Two wires have lengths, diameters and specific resistances all in the ratio of 1:2. The resistance of the first wire is 10 ohm. Resistance of the second wire in ohm will be

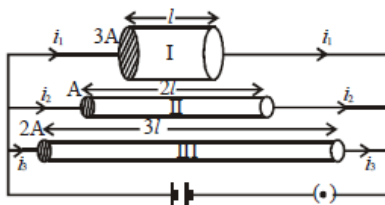
- (1) 5 (2) 10 (3) 20 (4) infinite
22. The length of a given cylindrical wire is increased by 100%. Due to the consequent decrease in diameter the change in the resistance of the wire will be
 (1) 200% (2) 100% (3) 50% (4) 300%
23. A wire has a resistance of 3.1Ω at 30°C and a resistance 4.5Ω at 100°C . The temperature coefficient of resistance of the wire
 (1) $0.0064 \text{ }^\circ\text{C}^{-1}$ (2) $0.0034 \text{ }^\circ\text{C}^{-1}$ (3) $0.0025 \text{ }^\circ\text{C}^{-1}$ (4) $0.0012 \text{ }^\circ\text{C}^{-1}$
24. The resistance of a wire at room temperature 30°C is found to be 10Ω . Now to increase the resistance by 10%, the temperature of the wire must be [The temperature coefficient of resistance of the material of the wire is 0.002 per $^\circ\text{C}$]
 (1) 36°C (2) 86°C (3) 63°C (4) 33°C
25. Two resistors A and B have resistances R_A and R_B respectively with $R_A < R_B$. The resistivities of their materials are ρ_A and ρ_B . Then
 (1) $\rho_A > \rho_B$ (2) $\rho_A = \rho_B$ (3) $\rho_A < \rho_B$
 (4) The information is not sufficient to find the relation between ρ_A and ρ_B .
26. A 6 volt battery is connected to the terminals of the three metre long wire of uniform thickness and resistance of 100 ohm. The difference of potential between two points on the wire separated by a distance of 50 cm will be
 (1) 1.5 volt (2) 3 volt (3) 3 volt (4) 1 volt
27. Two resistances R_1 and R_2 are made of different materials. The temperature coefficient of the material of R_1 is α and that of material of R_2 is $-\beta$. The resistance of the series combination of R_1 and R_2 will not change with temperature if $\frac{R_1}{R_2}$ equal to
 (1) $\frac{\alpha}{\beta}$ (2) $\frac{\alpha + \beta}{\alpha - \beta}$ (3) $\frac{\alpha^2 + \beta^2}{2\alpha\beta}$ (4) $\frac{\beta}{\alpha}$
28. The figure shows three conductors I, II and III of same material, different lengths l , $2l$ and $3l$ and of different areas of cross-section $3A$, A and $2A$ respectively. Arrange them in the increasing order of current drawn from battery.



- (1) $i_1 < i_2 < i_3$ (2) $i_3 < i_2 < i_1$ (3) $i_2 < i_1 < i_3$ (4) $i_2 < i_3 < i_1$

Topic 3: Combination of Resistors

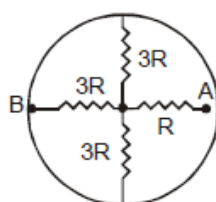
29. You have been provided with four 100 ohm resistors each with a tolerance of 2%. The number of ways in which these can be combined to have different equivalent resistances is
 (1) seven different combinations and seven different equivalents
 (2) eight different combinations and seven different equivalents resistances
 (3) nine different combinations and eight different resistances
 (4) ten different combinations and nine different resistances
30. In the network shown below, the ring has zero resistance. The equivalent resistance between the point A and B is




- (1) $2R$ (2) $4R$ (3) $7R$ (4) $10R$
31. You are given two resistances R_1 and R_2 . By using them singly, in series and in parallel, you can obtain four resistances of 1.5Ω , 2Ω , 6Ω and 8Ω . The values of R_1 and R_2 are

- (1) 1Ω , 7Ω (2) 1.5Ω , 6.5Ω (3) 3Ω , 5Ω (4) 2Ω , 6Ω

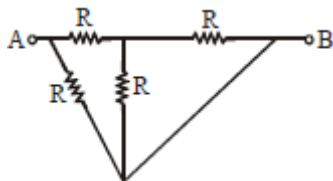32. The equivalent resistance between points A and B is




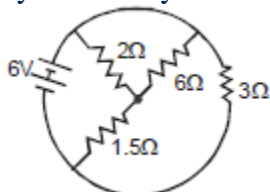- (1) $2R$ (2) $(3/4)R$ (3) $(4/3)R$ (4) $(3/5)R$
33. The total current supplied to the circuit by the battery is



- (1) $4A$ (2) $2A$ (3) $1A$ (4) $6A$
34. A letter 'A' is constructed of a uniform wire with resistance 1.0Ω per cm, The sides of the letter are 20 cm and the cross piece in the middle is 10 cm long. The apex angle is 60° . The resistance between the ends of the legs is close to:

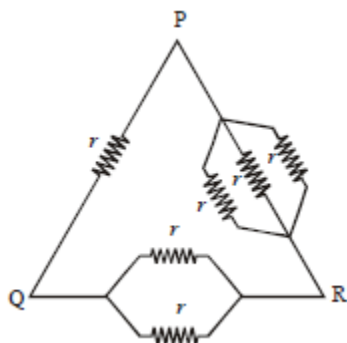
- (1) 50.0Ω (2) 10Ω (3) 36.7Ω (4) 26.7Ω
35. Six equal resistances are connected between points P, Q and R as shown in figure. Then net resistance will be maximum between:



- (1) P and R (2) P and Q (3) Q and R (4) Any two points
36. Two metal wires of identical dimension are connected in series. If σ_1 and σ_2 are the conductivities of the metal wires respectively, the effective conductivity of the combination is:

- (1) $\frac{\sigma_1 + \sigma_2}{2\sigma_1\sigma_2}$ (2) $\frac{\sigma_1 + \sigma_2}{\sigma_1\sigma_2}$ (3) $\frac{\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$ (4) $\frac{2\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$

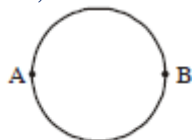37. A wire of resistance 12 ohms per meter is bent to form a complete circle of radius 10 cm. The resistance between its two diametrically opposite points, A and B as shown in the figure, is




- (1) 3Ω (2) $6\pi\Omega$ (3) 6Ω (4) $0.6\pi\Omega$
38. Three resistances each of 4Ω are connected to form a triangle. The resistance between any two terminals is

- (1) 12Ω (2) 2Ω (3) 6Ω (4) $8/3\Omega$
39. Two wires of the same metal have same length, but their cross-sections are in the ratio 3:1. They are joined in series. The resistance of thicker wire is 10Ω . The total resistance of the combination will be

- (1) $10\ \Omega$ (2) $20\ \Omega$ (3) $40\ \Omega$ (4) $100\ \Omega$


Topic 4: Kirchoff's Laws and Cells

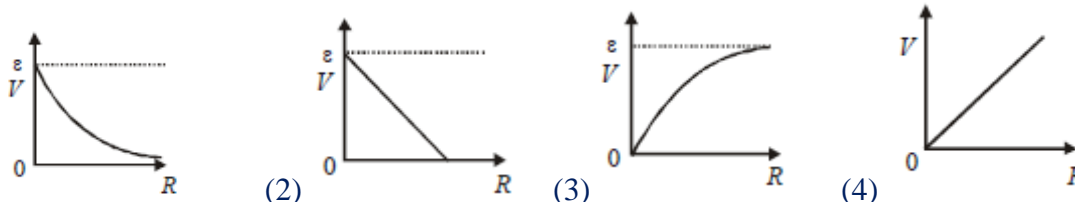40. Kirchoff's first law, i.e., $\sum i = 0$ at a junction, deals with the conservation of
 (1) charge (2) energy (3) momentum (4) angular momentum
41. A battery of emf 10V and internal resistance $30\ \text{hm}$ is connected to a resistor. The current in the circuit is 0.5 amp. The terminal voltage of the battery when the circuit is closed is
 (1) 10V (2) zero (3) 1.5V (4) 8.5V
42. Five cells each of emf E and internal resistance r send the same amount of current through an external resistance R whether the cells are connected in parallel or in series. Then the ratio $\left(\frac{R}{r}\right)$ is
 (1) 2 (2) $1/2$ (3) $1/5$ (4) 1
43. Cell having an emf e and internal resistance r is connected across a variable external resistance R . As the resistance R is increased, the plot of potential difference V across R is given by :




44. The potential difference between the terminals of a cell in an open circuit is 2.2 V. When a resistor of $5\ \Omega$ is connected across the terminals of the cell, the potential difference between the terminals of the cell is found to be 1.8 V. The internal resistance of the cell is
 (1) $\frac{7}{12}\ \Omega$ (2) $\frac{10}{9}\ \Omega$ (3) $\frac{9}{10}\ \Omega$ (4) $\frac{12}{7}\ \Omega$

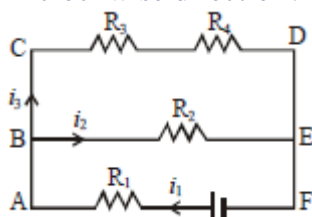
45. Which of the following is the correct equation when Kirchoff's loop rule is applied to the loop BCDEB in clockwise direction?



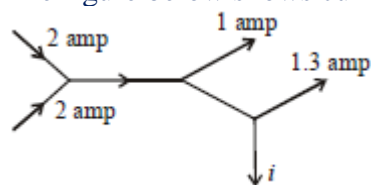- (1) $-i_3R_3 - i_3R_4 - i_2R_2 = 0$
 (2) $-i_3R_3 - i_3R_4 + i_2R_2 = 0$
 (3) $-i_3R_3 + i_3R_4 + i_2R_2 = 0$
 (4) $i_3R_3 + i_3R_4 + i_2R_2 = 0$
46. The figure below shows currents in a part of electric circuit. The current i is



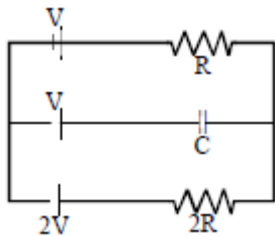- (1) 1.7 amp (2) 3.7 amp (3) 1.3 amp (4) 1 amp
47. In the circuit shown in figure, with steady current, the potential drop across the capacitor must be




- (1) V (2) $V/2$ (3) $V/3$ (4) $2V/3$

Topic 5: Electrical Energy, Power and Heating Effect of Current

48. A heater of 220 V heats a volume of water in 5 minutes. The same heater when connected to 110 V heats the same volume of water in (minutes)

- (1) 5 (2) 20 (3) 10 (4) 2.5

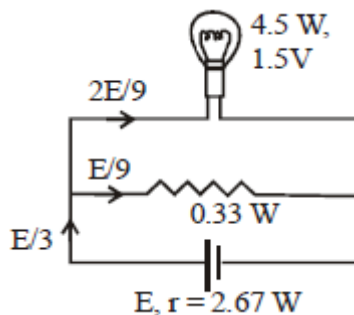49. A torch bulb rated as 4.5 W, 1.5 V is connected as shown in fig. The e.m.f. of the cell, needed to make the bulb glow at full intensity is




- (1) 4.5 V (2) 1.5 V (3) 2.67 V (4) 13.5 V

50. A electric tea kettle has two heating coils. When first coil of resistance R_1 is switched on, the kettle begins to boil tea in 6 minutes. When second coil of resistance R_2 is switched on, the boiling begins in 8 minutes. The value of R_1/R_2 is

- (1) $3/7$ (2) $7/3$ (3) $4/3$ (4) $3/4$

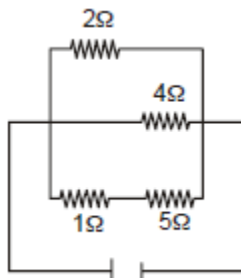51. A current of 3 amp flows through the 2Ω resistor shown in the circuit. The power dissipated in the 5Ω resistor is:



- (1) 4 watt (2) 2 watt (3) 1 watt (4) 5 watt

52. The resistance of hot tungsten filament is about 10 times the cold resistance. What will be the resistance of 100Ω and 200 V lamp when not in use?

- (1) 20Ω (2) 40Ω (3) 200Ω (4) 400Ω

53. Ten identical cells connected in series are needed to heat a wire of length one meter and radius ' r ' by 10°C in time ' t '. How many cells will be required to heat the wire of length two meter of the same radius by the same temperature in time ' t '?

- (1) 10 (2) 20 (3) 30 (4) 40


54. Two 220 volt, 100 watt bulbs are connected first in series and then in parallel. Each time the combination is connected to a 220 volt a.c. supply line. The power drawn by the combination in each case respectively will be

- (1) 50 watt, 200 watt (2) 50 watt, 100 watt
 (3) 100 watt, 50 watt (4) 200 watt, 150 watt


55. A 100-W bulb and a 25-W bulb are designed for the same voltage. They have filaments of the same length and material. The ratio of the diameter of the 100-W bulb to that of the 25-W bulb is
 (1) 4 : 1 (2) 2 : 1 (3) $\sqrt{2}$: 1 (4) 1 : 2
56. Water boils in the electric kettle in 15 minutes after switching on. If the length of heating wire is decreased to $\frac{2}{3}$ of its initial value, then the same amount of water will boil with the same supply voltage in
 (1) 8 minutes (2) 10 minutes (3) 12 minutes (4) 15 minutes

Topic 6: Wheatstone Bridge and Different Measuring Instruments

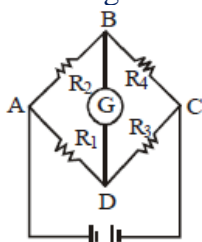
57. In a meter bridge experiment null point is obtained at 20 cm. from one end of the wire when resistance X is balanced against another resistance Y . If $X < Y$, then where will be the new position of the null point from the same end, if one decides to balance a resistance of $4X$ against Y
 (1) 40 cm (2) 80 cm (3) 50 cm (4) 70 cm
58. The current in the primary circuit of a potentiometer is 0.2 A. The specific resistance and cross-section of the potentiometer wire are 4×10^{-7} ohm metre and 8×10^{-7} m², respectively. The potential gradient will be equal to
 (1) 1 V/m (2) 0.5 V/m (3) 0.1 V/m (4) 0.2 V/m
59. The resistance of an ammeter is 13Ω and its scale is graduated for a current upto 100 amps. After an additional shunt has been connected to this ammeter it becomes possible to measure currents upto 750 amperes by this meter. The value of shunt-resistance is
 (1) 2Ω (2) 0.2Ω (3) $2 \text{ k}\Omega$ (4) 20Ω
60. In the figure in balanced condition of Wheatstone bridge



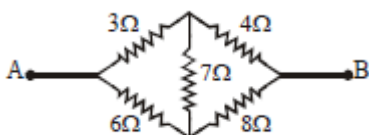- (1) B is at higher potential.
 (2) D is at higher potential.
 (3) Any of the two B or D can be at higher potential than other arbitrarily.
 (4) B and D are at same potential.
61. Five resistances have been connected as shown in the figure. The effective resistance between A and B is




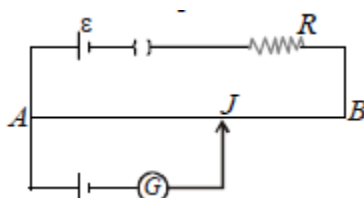- (1) $\frac{14}{3} \Omega$ (2) $\frac{20}{3} \Omega$ (3) 14Ω (4) 21Ω
62. AB is a wire of potentiometer with the increase in value of resistance R , the shift in the balance point J will be




- (1) towards B
 (2) towards A
 (3) remains constant
 (4) first towards B then back towards A
63. 125 cm of potentiometer wire balances the emf. of a cell and 100 cm of the wire is required for balance, if the poles of the cell are joined by a 2Ω resistor. Then the internal resistance of the cell is

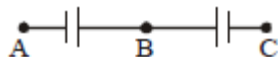- (1) 0.25Ω (2) 0.5Ω (3) 0.75Ω (4) 1.25Ω
64. A potentiometer is connected across A and B and a balance is obtained at 64.0 cm. When the potentiometer lead at B is moved to C, a balance is found at 8.0 cm. If the potentiometer is now connected across B and C, a balance will be found at






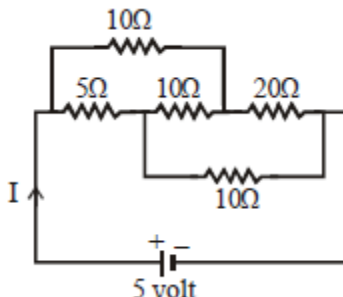
- (1) 8.0 cm (2) 56.0 cm (3) 64.0 cm (4) 72.0 cm
65. The current I drawn from the 5 volt source will be



- (1) 0.33 A (2) 0.5 A (3) 0.67 A (4) 0.17 A

NEET PREVIOUS YEARS QUESTIONS

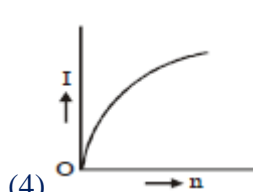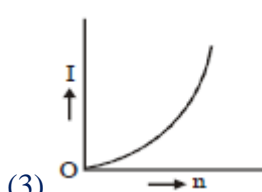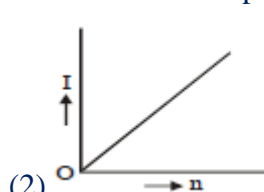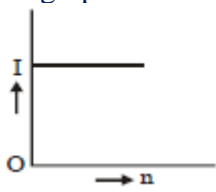1. A battery consists of a variable number 'n' of identical cells (having internal resistance 'r' each) which are connected in series. The terminals of the battery are short-circuited and the current I is measured. Which of the graphs shows the correct relationship between I and n ?



- (1) (2) (3) (4)

2. A set of 'n' equal resistors, of value 'R' each, are connected in series to a battery of emf 'E' and internal resistance 'R'. The current drawn is I . Now, the 'n' resistors are connected in parallel to the same battery. Then the current drawn from battery becomes $10 I$. The value of 'n' is

- (1) 10 (2) 11 (3) 9 (4) 20

3. A carbon resistor of $(47 \pm 4.7) \text{ kW}$ is to be marked with rings of different colours for its identification. The colour code sequence will be [2018]

- (1) Violet – Yellow – Orange – Silver
 (2) Yellow – Violet – Orange – Silver
 (3) Green – Orange – Violet – Gold
 (4) Yellow – Green – Violet – Gold

4. The resistance of a wire is 'R' ohm. If it is melted and stretched to 'n' times its original length, its new resistance will be :

- (1) $\frac{R}{n}$ (2) $n^2 R$ (3) $\frac{R}{n^2}$ (4) nR

5. A potentiometer is an accurate and versatile device to make electrical measurements of E.M.F. because the method involves

- (1) Potential gradients
 (2) A condition of no current flow through the galvanometer
 (3) A combination of cells, galvanometer and resistances
 (4) Cells

6. A potentiometer wire is 100 cm long and a constant potential difference is maintained across it. Two cells are connected in series first to support one another and then in opposite direction. The balance points are obtained at 50 cm and 10 cm from the positive end of the wire in the two cases. The ratio of emf's is:

- (1) 5 : 1 (2) 5 : 4 (3) 3 : 4 (4) 3 : 2


7. The charge flowing through a resistance R varies with time t as $Q = at - bt^2$, where a and b are positive constants. The total heat produced in R is:

- (1) $\frac{a^3R}{6b}$ (2) $\frac{a^3R}{3b}$ (3) $\frac{a^3R}{2b}$ (4) $\frac{a^3R}{b}$

8. A circuit contains an ammeter, a battery of 30V and a resistance 40.8Ω all connected in series. If the ammeter has a coil of resistance 480Ω and a shunt of 20Ω , the reading in the ammeter will be:


- (1) 0.25 A (2) 2A (3) 1 A (4) 0.5 A

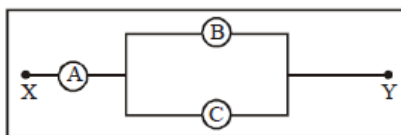9. A, B and C are voltmeters of resistance R, 1.5 R and 3R respectively as shown in the figure. When some potential difference is applied between X and Y, the voltmeter readings are V_A , V_B and V_C respectively. Then [2015]



- (1) $V_A \neq V_B = V_C$
 (2) $V_A = V_B \neq V_C$
 (3) $V_A \neq V_B \neq V_C$
 (4) $V_A = V_B = V_C$

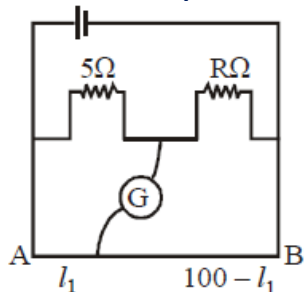10. The resistances in the two arms of the meter bridge are 5Ω and $R\Omega$, respectively. When the resistance R is shunted with an equal resistance, the new balance point is at $1.6 l_1$. The resistance 'R' is :




- (1) 10Ω (2) 15Ω (3) 20Ω (4) 25Ω

11. Two cities are 150 km apart. Electric power is sent from one city to another city through copper wires. The fall of potential per km is 8 volt and the average resistance per km is 0.5Ω . The power loss in the wires is :


- (1) 19.2 W (2) 19.2 kW (3) 19.2 J (4) 12.2 kW

12. Six similar bulbs are connected as shown in the figure with a DC source of emf E, and zero internal resistance. The ratio of power consumption by the bulbs when

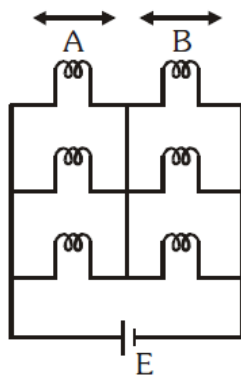
- (i) all are glowing and
 (ii) in the situation when two from section A and one from section B are glowing, will be :



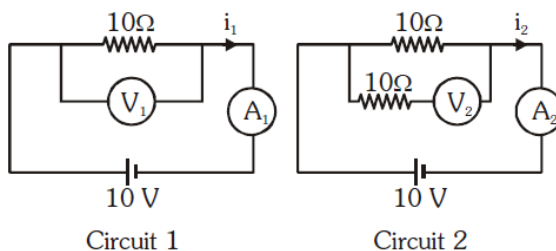
- (1) 4 : 9 (2) 9 : 4 (3) 1 : 2 (4) 2 : 1
13. Which of the following acts as a circuit protection device?
 (1) conductor (2) inductor (3) switch (4) fuse
14. In the circuits shown below, the readings of the voltmeters and the ammeters will be :



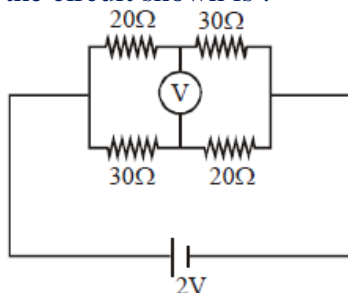
- (1) $V_2 > V_1$ and $i_1 = i_2$ (2) $V_1 = V_2$ and $i_1 > i_2$
 (3) $V_1 = V_2$ and $i_1 = i_2$ (4) $V_2 > V_1$ and $i_1 > i_2$
15. The reading of an ideal voltmeter in the circuit shown is :



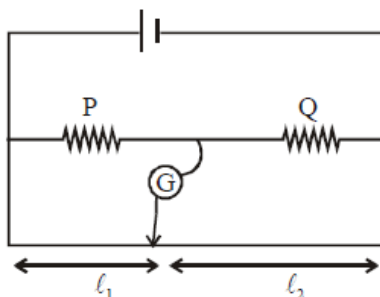
- (1) 0.6 V (2) 0 V (3) 0.5 V (4) 0.4 V
16. The metre bridge shown is in balanced position with $\frac{P}{Q} = \frac{l_1}{l_2}$. If we now interchange the positions of galvanometer and cell, will the bridge work ? If yes, what will be balance condition ?



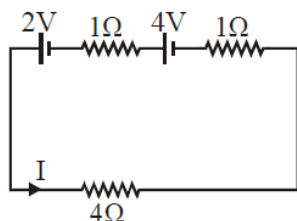
- 1) yes, $\frac{P}{Q} = \frac{l_2 - l_1}{l_2 + l_1}$ 2) no, no null point 3) yes, $\frac{P}{Q} = \frac{l_2}{l_1}$ 4) yes, $\frac{P}{Q} = \frac{l_1}{l_2}$
17. For the circuit shown in the figure, the current I will be



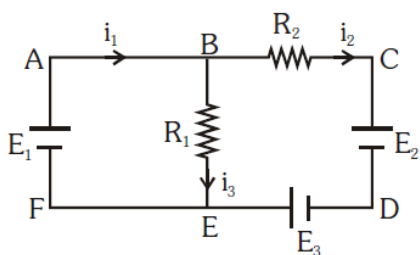
- (1) 0.75 A (2) 1 A (3) 1.5 A (4) 0.5 A
18. Two solid conductors are made up of same material, have same length and same resistance. One of them has a circular cross section of area A_1 and the other one has a square cross section of area A_2 . The ratio A_1/A_2 is
 (1) 1.5 (2) 1 (3) 0.8 (4) 2
19. For the circuit given below, the Kirchoff's loop rule for the loop BCDEB is given by the equation



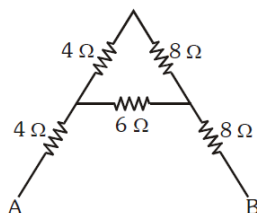
- (1) $-i_2R_2 + E_2 - E_3 + i_3R_1 = 0$
 (2) $i_2R_2 + E_2 - E_3 - i_3R_1 = 0$
 (3) $i_2R_2 + E_2 + E_3 + i_3R_1 = 0$
 (4) $-i_2R_2 + E_2 + E_3 + i_3R_1 = 0$
20. The equivalent resistance between A and B for the mesh shown in the figure is




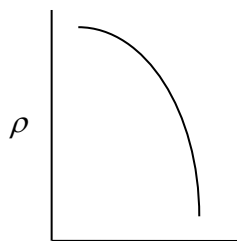
- (1) 7.2Ω (2) 16Ω (3) 30Ω (4) 4.8Ω
21. Which of the following graph represents the variation of resistivity (ρ) with temperature (T) for copper?



1)

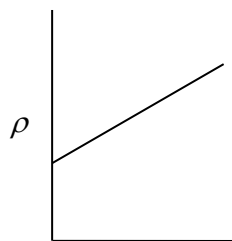

2)

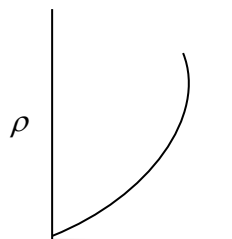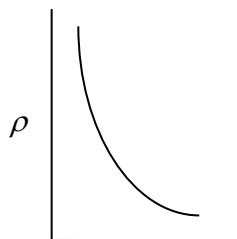

3)

T

4)

T

22. A resistance wire connected in the left gap of a metre bridge balances a $10\ \Omega$ resistance in the right gap at a point which divides the bridge wire in the ratio 3 : 2. If the length of the resistance wire is 1.5m. Then the length of $1\ \Omega$ of the resistance wire is

- 1) $1.5 \times 10^{-2} m$ 2) $1.0 \times 10^{-2} m$ 3) $1.0 \times 10^{-1} m$ 4) $1.5 \times 10^{-1} m$

23. A charged particle having drift velocity of $7.5 \times 10^{-4} ms^{-1}$ in an electric field of $3 \times 10^{10} Vm^{-1}$, has a mobility in $m^2V^{-1}s^{-1}$ of:

- 1) 2.25×10^{-15} 2) 2.25×10^{15} 3) 2.5×10^6 4) 2.5×10^{-6}

24. The color code of a resistance is given below



The values of resistance and tolerance, respectively, are

- 1) $470\ \Omega$, 5% 2) $470\ k\Omega$, 5% 3) $47\ k\Omega$, 10% 4) $4.7\ k\Omega$, 5%

25. The solids which have the negative temperature coefficient of resistance are

- 1) insulators and semiconductors 2) metals
3) Insulators only 4) Semiconductors only

26. Column-I gives certain physical terms associated with flow of current through a metallic conductor. Column – II gives some mathematical relations involving electrical quantities. Match Column – I and Column – II with appropriate relations.

Column-I

(1) Drift Velocity

(2) Electrical Resistivity

(3) Relaxation Period

(4) Current Density

1) (1)-I, (2)-(S), (3)-(Q), (4)-(P)

3) (1)-I, (2)-(P), (3)-(S), (4)-(P)

Column-II

P) $\frac{m}{ne^2\rho}$

Q) nev_d

R) $\frac{eE}{m}\tau$

S) $\frac{E}{J}$

2) (1)-I, (2)-(P), (3)-(S), (4)-(Q)

4) (1)-I, (2)-(S), (3)-(P), (4)-(Q)


27. In a potentiometer circuit a cell of EMF 1.5V gives balance point at 36 cm length of wire. If another cell of EMF 2.5 V replaces the first cell, then at what length of the wire, the balance point occurs?

- 1) 21.6 cm 2) 64 cm 3) 62 cm 4) 60 cm

28. The effective resistance of a parallel connection that consists of four wires of equal length, equal area of cross-section and same material is $0.25\ \Omega$. What will be the effective resistance if they are connected in series?

- 1) $0.5\ \Omega$ 2) $1\ \Omega$ 3) $4\ \Omega$ 4) $0.25\ \Omega$

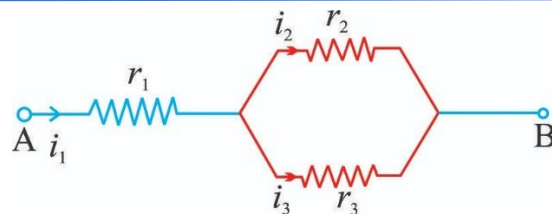29. Three resistors having resistances r_1 , r_2 and r_3 are connected as shown in the given circuit. The ratio $\frac{i_2}{i_1}$ of currents in terms of resistances used in the circuit is



- 1) $\frac{r_2}{r_2 + r_3}$ 2) $\frac{r_1}{r_1 + r_2}$ 3) $\frac{r_2}{r_1 + r_3}$ 4) $\frac{r_2}{r_2 + r_3}$


30. A copper wire of length 10 m and radius $(10^{-2} / \sqrt{\pi})$ m has electrical resistance of 10Ω . The current density in the wire for an electric field strength of $10(\text{V} / \text{m})$ is:

- 1) 10^4 A/m^2 2) 10^6 A/m^2 3) 10^{-5} A/m^2 4) 10^5 A/m^2

31. Two resistors of resistance 100Ω and 200Ω are connected in a parallel in an electrical circuit the ratio of the thermal energy developed in 100Ω to that in 200Ω in a given time is:

- (1) 1 : 2 (2) 2 : 1 (3) 1 : 4 (4) 4 : 1

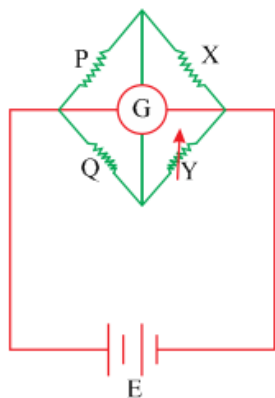32. A Wheatstone bridge is used to determine the value of unknown resistance X by adjusting the variable resistance Y as shown in the figure. For the most precise measurement of X, the resistances P and Q



- 1) should be approximately equal to $2X$
 2) should be approximately equal and are small
 3) should be very large and unequal
 4) do not play any significant role

NCERT LINE BY LINE QUESTIONS – ANSWERS

1) b	2) d	3) b	4) c	5) d
6) b	7) c	8) d	9) c	10) d
11) d	12) a	13) a	14) b	15) b
16) d	17) c	18) b	19) b	20) c
21) c	22) b	23) a	24) d	25) a
26) d	27) c	28) a	29) b	30) d
31) a	32) d	33) c	34) b	35) c
36) c	37) c	38) b	39) a	40) d
41) d	42) a	43) b	44) b	45) c
46) c	47) b	48) a	49) b	50) a
51) c	52) b	53) b	54) b	55) b
56) c	57) b	58) b	59) c	60) b
61) c	62) a	63) a	64) d	65) b
66) B	67) B	68) A	69) A	70) D
71) D	72) A	73) B	74) A	75) B
76) A	77) B	78) B	79) A	80) B
81) A	82) B	83) B	84) A	

TOPIC WISE PRACTICE QUESTIONS - ANSWERS

1) 4	2) 3	3) 4	4) 3	5) 3	6) 3	7) 4	8) 1	9) 2	10) 2
11) 2	12) 2	13) 3	14) 3	15) 1	16) 2	17) 2	18) 2	19) 4	20) 3
21) 2	22) 4	23) 1	24) 2	25) 4	26) 4	27) 4	28) 4	29) 4	30) 1
31) 4	32) 4	33) 1	34) 4	35) 2	36) 4	37) 1	38) 4	39) 3	40) 1
41) 4	42) 4	43) 3	44) 2	45) 2	46) 1	47) 3	48) 2	49) 4	50) 3
51) 4	52) 2	53) 2	54) 1	55) 2	56) 2	57) 3	58) 3	59) 1	60) 4
61) 1	62) 1	63) 2	64) 2	65) 2					

NEET PREVIOUS YEARS QUESTIONS-ANSWERS

1) 1	2) 1	3) 2	4) 2	5) 2	6) 4	7) 1	8) 4	9) 4	10) 2
11) 1	12) 2	13) 4	14) 3	15) 4	16) 4	17) 2	18) 2	19) 2	20) 2
21) 4	22) 3	23) 3	24) 1	25) 1	26) 4	27) 4	28) 3	29) 1	30) 4
31) 2	32) 2								

TOPIC WISE PRACTICE QUESTIONS - SOLUTIONS

1. (4) $I = ne = 10^6 \times 1.6 \times 10^{-19} = 1.6 \times 10^{-13} \text{ A}$
2. (3) The value of drift velocity of electrons = 10^{-5} m/s and that of thermal velocity = 10^5 m/s .
3. (4) $v_d = \frac{1}{nAe} = \frac{j}{ne} = \left(\frac{\sigma}{ne} \right) E \Rightarrow v_d \propto E$
4. (3) Current $I = \frac{\text{Charge}}{\text{Time}}$
as charge $q = n \times 1.6 \times 10^{-19}$

$$10^{-3} \text{ amp} = \frac{n \times 1.6 \times 10^{-19}}{1 \text{ sec}} \Rightarrow n = 6.25 \times 10^{15}$$

5. (3) $v_d = \frac{I}{neA} = \frac{24 \times 10^{-3}}{3 \times 10^{23} \times 1.6 \times 10^{-19} \times 10^{-4}} = 5 \times 10^{-3} \text{ m/sec}$

6. (3) $v_d = \frac{I}{neA}$ Here, $I = 5.4 \text{ A}$, $n = 8.4 \times 10^{28}$, per m^3

$$A = 10^{-6} \text{ m}^2, e = 1.6 \times 10^{-19} \text{ C}$$

$$\therefore v_d = \frac{5.4}{8.4 \times 10^{28} \times 1.6 \times 10^{-19} \times 10^{-6}} = 0.4 \text{ mm/s}$$

7. (4) $I = neAv_d = 2 \times 10^{21} \times 1.6 \times 10^{-19} \times 10 \times 0.25 \times 10^{-3}$
 $= 2 \times 1.6 \times 0.25 = \frac{8}{10} = 0.8 \text{ A}$

8. (1) Current flowing through the conductor,
 $I = n e v A$. Hence

$$\frac{4}{1} = \frac{nev_{d_1} \pi(1)^2}{nev_{d_2} \pi(2)^2} \text{ or } \frac{v_{d_1}}{v_{d_2}} = \frac{4 \times 4}{1} = \frac{16}{1}$$

9. (2) Electron density, $n = \frac{d \times N}{M}$

$$\text{So, } n = \frac{2.7 \times 10^3 \times 6.02 \times 10^{26}}{27}$$

$$= 6.02 \times 10^{28} \text{ electrons/m}^3$$

$$\therefore \text{Drift velocity} = 1.29 \times 10^{-4} \text{ m/s}$$

10. (2) $J = I/A = 10^{-4} / (0.30 \times 0.50)$

$$= 6.7 \times 10^{-4} \text{ Cm}^{-2} / \text{s} = 6.7 \times 10^{-4} \text{ Am}^{-2}$$

11. (2) Current $I = (2.9 \times 10^{28} + 1.2 \times 10^{18}) \times 1.6 \times 10^{-19}$ towards right

12. (2) Current density $J = I/A$
 $= 50 \times 16^{-6} / 50 \times 10^{-6} = 1 \text{ Am}^{-2}$

13. (3) $v_d = \frac{J}{ne} \Rightarrow v_d \propto J$ (current density)

$$J_1 = \frac{i}{A} \text{ and } J_2 = \frac{2i}{2A} = \frac{1}{A} J_1;$$

$$\therefore (v_d)_1 = (v_d)_2 = v$$

14. (3) $R = \frac{\rho \ell_1}{A_1}$, now $\ell_2 = 2\ell_1$

$$A_2 = \pi(r_2)^2 = \pi(2r_1)^2 = 4\pi r_1^2 = 4A_1$$

$$\therefore R_2 = \frac{\rho(2\ell_1)}{4A_1} = \frac{\rho \ell_1}{2A_1} = \frac{R}{2}$$

\therefore Resistance is halved, but specific resistance remains the same.

15. (1) Since average drift velocity $= \frac{1}{2} \frac{eE}{m} \times (\tau)$

$$\text{Now, } I = NeA \times (\text{avg. drift velocity})$$

$$= \frac{ne^2 AE}{2m\ell} \times \tau = \frac{Ne^2 AV}{2m\ell} \times \tau$$

$$R = \frac{V}{I} = \frac{m\ell}{Ne^2 \tau A^2}, \text{ where } N \text{ is electron density.}$$

16. (2) The figure is showing $I - V$ characteristics of non ohmic or non-linear conductors.

17. (2) Given : Length of wire (l) = 15m

$$\text{Area (1)} = 6 \times 10^{-7} \text{ m}^2$$

$$\text{Resistance (R)} = 5 \text{ W.}$$

We know that resistance of the wire material

$$R = \rho \frac{l}{A} \Rightarrow 5 = \rho \times \frac{15}{6 \times 10^{-7}} = 2.5 \times 10^7 \rho$$

$$\Rightarrow \rho = \frac{5}{2.5 \times 10^7} = 2 \times 10^{-7} \Omega - m$$

18. (2) Given $\frac{m_1}{m_2} = \frac{2}{3}, \frac{l_1}{l_2} = \frac{3}{4}$

$$\frac{m_1}{m_2} = \frac{2}{3} = \frac{A_1 l_1 d}{A_2 l_2 d} \Rightarrow \frac{2}{3} = \frac{A_1}{A_2} \times \frac{3}{4} \therefore \frac{A_1}{A_2} = \frac{8}{9}$$

As we know,

$$R = \rho \frac{l}{A} \frac{R_1}{R_2} = \frac{l_1}{A_1} \times \frac{A_2}{l_2} = \frac{3}{4} \times \frac{9}{8} = \frac{27}{32}; R_1 : R_2 = 27 : 32$$

19. (4) $m = \ell \times \text{area} \times \text{density}$

$$\text{Area} \propto \frac{m}{\ell}$$

$$R \propto \frac{l}{\text{Area}} \propto \frac{l^2}{m}$$

$$R_1 : R_2 : R_3 = \frac{l_1^2}{m_1} : \frac{l_2^2}{m_2} : \frac{l_3^2}{m_3}$$

$$R_1 : R_2 : R_3 = \frac{25}{1} : \frac{9}{3} : \frac{1}{5} = 125 : 15 : 1$$

20. (3) Since $R = \frac{\rho \ell}{A} = \frac{\rho \ell}{\pi (d/2)^2} = \frac{4\rho \ell}{\pi d^2}$

If ℓ becomes $\ell/2$ & d becomes $2d$, the new resistance is

$$R' = \frac{\rho \ell / 2}{\pi (2d/2)^2} = \frac{\rho \ell}{2 \times \pi d^2} = \frac{R}{8}$$

21. (2) Resistance of the wire $R = \rho \frac{l}{A}$, where $A = \frac{\pi d^2}{4}$

$$\Rightarrow \frac{R_2}{R_1} = \frac{\rho_2 l_2 d_1^2}{\rho_1 l_1 d_2^2}$$

$$\therefore \frac{R_2}{10} = \frac{1}{2} \times \frac{1}{2} \times \frac{2^2}{1^2} = 1$$

$$\Rightarrow R_2 = 10 \Omega$$

22. (4) Here the total volume of the wire is constant .

$$\text{Resistance } R = \frac{\rho l^2}{V} \text{ or } R \propto l^2$$

let, initial length $l_1 = l_0$ and final length $l_2 = l_0 + l_0 \times \frac{100}{100} = 2l_0$

$$\frac{R_2}{R_1} = \frac{l_2^2}{l_1^2} = \frac{4l_0^2}{l_0^2} = 4$$

$$\text{The change in resistance} = \frac{R_2 - R_1}{R_1} \times 100 = \left[\frac{R_2}{R_1} - 1 \right] 100 = (4 - 1)100 = 300\%$$

23. (1) $R_1 = 3.1 \Omega$ at $t = 30^\circ C$

$$R_2 = 4.5 \Omega \text{ at } t = 100^\circ C$$

$$\text{We have, } R = R_0(1 + \alpha t)$$

$$\therefore R_1 = R_0[1 + \alpha(30)]$$

$$R_2 = R_0[1 + \alpha(100)]$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{1 + 30\alpha}{1 + 100\alpha} \Rightarrow \frac{3.1}{4.5} = \frac{1 + 30\alpha}{1 + 100\alpha} \Rightarrow \alpha = 0.0064^\circ C^{-1}$$

24. (2) $R_t = R_0(1 + \alpha t)$

$$\text{Initially, } R_0(1 + 30\alpha) = 10 \Omega$$

$$\text{Finally, } R_0(1 + \alpha t) = 11 \Omega$$

$$= \frac{\rho l}{A}$$

25. (4) Resistance = $\frac{\rho l}{A}$, from this relation we can understand that the resistance also depends on length and area of the conductor. because in question it is not given that area and length are constant or any dependence of them over resistance. So we cannot deduce the values of resistivity directly from the values of the resistance.

26. (4) $R \propto l$

$$\text{For } 300 \text{ cm, } R = 100 \Omega$$

$$\text{For } 50 \text{ cm, } R^l = \frac{100}{300} \times 50 = \frac{50}{3} \Omega$$

$$\therefore IR = 6 \Rightarrow IR^l = \frac{6}{R} \times R^l = \frac{6}{100} \times \frac{50}{3} = 1 \text{ volt}$$

27. (4) $R_1 + R_2 = \text{Constant}$, R_1 will increase, R_2 will decrease.

$$R_1 \alpha \Delta T - R_2 \beta \Delta T = 0 \Rightarrow R_1 \alpha \Delta T = R_2 \beta \Delta T$$

$$\therefore \frac{R_1}{R_2} = \frac{\beta}{\alpha}$$

28. (4) $i_2 < i_3 < i_1$

29. (4) ten different combinations and nine different resistances

30. (1) As the ring has no resistance, the three resistances of $3R$ each are in parallel.

$$\Rightarrow \frac{1}{R^l} = \frac{1}{3R} + \frac{1}{3R} + \frac{1}{3R} = \frac{1}{R} \Rightarrow R^l = R$$

$$\therefore \text{between point A and B equivalent resistance} = R + R = 2R.$$

31. (4) $R_1 = 2 \Omega$ and $R_2 = 6 \Omega$

$$\text{In series, } R = R_1 + R_2 = 8 \Omega$$

In parallel, $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{2} + \frac{1}{6} = \frac{4}{6}$

$\therefore R = \frac{6}{4} = 1.5\Omega$

\therefore We can get $1.5\Omega, 2\Omega, 6\Omega$ and 8Ω resistors by 2Ω and 6Ω resistors.

32. (4) Formula for equivalent resistance in series $R=R_1+R_2$

Formula for equivalent resistance in parallel $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$

Now, given circuit can be rearrange as in figure 2

Using formula for equivalent resistance in parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


Equivalent resistance between B and C = $\frac{R}{2}$

and it is in series with resistance(AC), So resistance of lower branch = $\frac{3R}{2}$

Now, equivalent resistance between A and B

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{2}{3R} \Rightarrow R_{eq} = \frac{3R}{5}$$

33. (1)

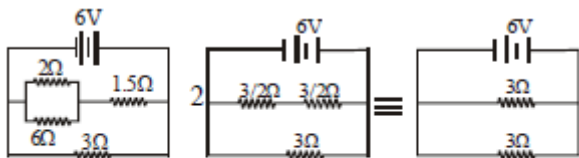

hence $R_{eq} = 3/2; \therefore I = \frac{6}{3/2} = 4A$

34. (4) For ADE $\frac{1}{R^1} = \frac{1}{2x} + \frac{1}{10}$ or $R^1 = \frac{20x}{10+2x}$

$R_{BC} = \frac{20x}{10+2x} + 20 - x + 20 - x$ -----(i)

or $\frac{20x}{10+2x} + 40 = 2x$

Solving we get $x = 10\Omega$

Putting the value of $x = 10\Omega$ in equation (i)

We get

$R_{BC} = \frac{20 \times 10}{10 + 2 \times 10} + 20 - 10 + 20 - 10 = \frac{80}{3} = 26.7\Omega$


35. (2) The combination of resistances is shown in figure.

Maximum resistance will be between P and Q.

$$R_{PQ} = \frac{R \left(\frac{R}{3} + \frac{R}{2} \right)}{R + \frac{R}{3} + \frac{R}{2}} = \frac{5R^2/6}{11R/6} = \frac{5R}{11}$$


$$R_{QR} = \frac{\frac{R}{2} \left(R + \frac{R}{3} \right)}{11R/6} = \frac{2R^2/3}{11R/6} = \frac{4R}{11}$$
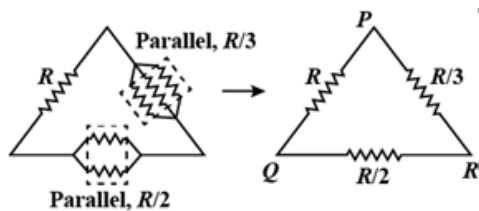
$$R_{PR} = \frac{\frac{R}{3} \left(R + \frac{R}{2} \right)}{11R/6} = \frac{R^2/2}{11R/6} = \frac{3R}{11}$$



Hence, the maximum value lies between P and Q.

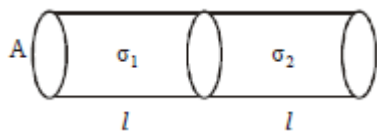
36. (4) In figure, two metal wires of identical dimension are connected in series



$$R_{eq} = \frac{l}{\sigma_1 A} + \frac{l}{\sigma_2 A} = \frac{l_{eq}}{\sigma_{eq} A_{eq}}$$

$$\frac{2l}{\sigma_{eq} A} = \frac{l}{A} \left(\frac{\sigma_1 + \sigma_2}{\sigma_1 \sigma_2} \right) \therefore \sigma_{eq} = \frac{2\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$$


37. (1)

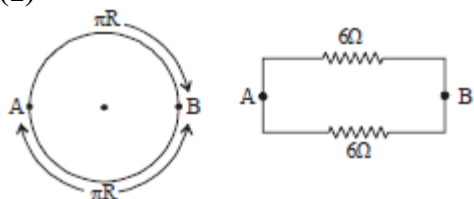

The resistance of length $2\pi R$ is 12Ω . Hence the resistance of length πR is 6Ω . Thus two resistances of 6Ω can be represented as shown in fig. 2.

$$\therefore \text{Equivalent resistance } R = \frac{6 \times 6}{12} = 3\Omega$$

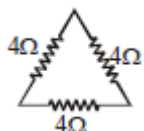38. (4) The two resistances are connected in series and the resultant is connected in parallel with the third resistance.



$$\therefore R^{\parallel} = 4\Omega + 4\Omega = 8\Omega \text{ and } \frac{1}{R^{\parallel}} = \frac{1}{8} + \frac{1}{4} = \frac{3}{8} \text{ or } R^{\parallel} = \frac{8}{3}\Omega$$

39. (3) Length of each wire = ℓ ; Area of thick wire (A_1) = $3A$; Area of thin wire (A_2) = A and resistance of

thick wire (R_1) = 10Ω . Resistance (R) = $\rho \frac{\ell}{A} \propto \frac{1}{A}$ (if ℓ is constant)

$$\therefore \frac{R_1}{R_2} = \frac{A_2}{A_1} = \frac{A}{3A} = \frac{1}{3} \text{ or } R_2 = 3R_1 = 3 \times 10 = 30\Omega$$

The equivalent resistance of these two resistors in series
 $= R_1 + R_2 = 30 + 10 = 40\Omega$

40. (1) Kirchoff's first law is based on the law of conservation of charge.

41. (4) Given: $E = 10V$, $r = 3\Omega$, $I = 0.5 A$, $R = ?$, $V = ?$

$$(i) \because I = \frac{E}{R+r}$$


$$\Rightarrow R+r = \frac{E}{I} = \frac{10}{0.5} = 20$$

$$\text{or } R = 20 - r$$

$$R = 20 - 3 = 17\Omega$$


$$(ii) V = IR = 0.5 \times 17 = 8.5 V$$

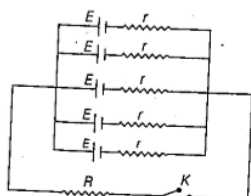42. (4) When 5 cells are joined in parallel as shown,



$$i = \frac{5E}{5R+r} \quad \dots(i)$$

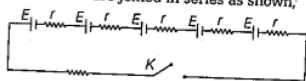When 5 cells are joined in series as shown,



$$i = \frac{\text{net emf}}{\text{total resistance}}$$

$$i = \frac{5E}{5R+r} \quad \dots(i)$$


When 5 cells are joined in series as shown,

$$i = \frac{5E}{5r+R}$$

So, according to the questions

$$i = \frac{5E}{5r+R} \text{ or } 4R = 4r \Rightarrow \frac{R}{r} = \frac{4}{4}; \frac{R}{r} = 1$$

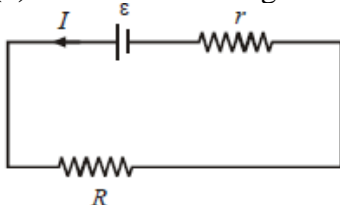
43. (3) The current through the resistance R



$$I = \left(\frac{\mathcal{E}}{R+r} \right)$$

The potential difference across R
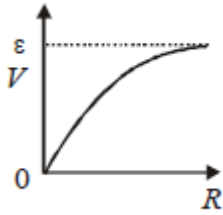
$$V = IR = \left(\frac{\mathcal{E}}{R+r} \right) R$$



$$V = \frac{\mathcal{E}}{\left(1 + \frac{r}{R} \right)}$$

when $R = 0$, $V = 0$, $R = \infty$, $V = \mathcal{E}$

Thus V increases as R increases upto certain limit, but it does not increase further.

44. (2) $E = V + ir$

$$2.2 = 1.8 + \frac{1.8}{5} \times r \Rightarrow r = \frac{10}{9} \Omega$$


45. (2) $-i_3 R_3 - i_3 R_4 + i_2 R_2 = 0$

46. (1) According to Kirchhoff's law

At junction A, $i_{AB} = 2 + 2 = 4$ A

At junction B, $i_{AB} = i_{BC} - 1 = 3$ A

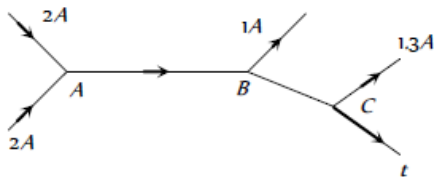At junction C, $i = i_{BC} - 1.3 = 3 - 1.3 = 1.7$ amp




47. (3) Applying Kirchhoff's law in BCDEFAB we get,

$$I = \frac{V}{3R}$$

Let A be at 0 V. Then potential at G is V.

Applying Kirchhoff's law for AFED, we get

$$0 + V + IR = V_D$$

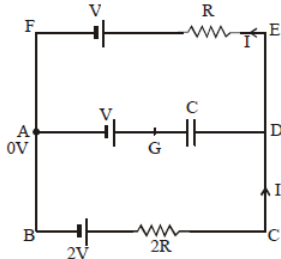

$$\therefore \text{potential different across capacitor} = \frac{4V}{3} - V = \frac{V}{3}$$

48. (2) $W = \text{Power} \times \text{time} = \frac{V^2 t}{R}$

R is the same.

$$\therefore V^2 t = \text{constant. } V_1^2 t_1 = V_2^2 t_2$$

$$220^2 \times 5 = 110^2 t_2$$

$$\therefore t_2 = 20 \text{ min}$$

49. (4) Resistance of bulb is $\frac{1.5 \times 1.5}{4.5} \Omega = 0.5 \Omega$

Resistance of parallel combination,

$$R = \frac{1 \times \frac{1}{2}}{1 + \frac{1}{2}} \Omega = \frac{1}{3} \Omega$$

Now, $r = \frac{E - V}{V} R \frac{8}{3} = \frac{E - 1.5}{1.5} \times \frac{1}{3}$ or $E = 13.5V$

50. (3) Heat supplied $= \frac{V^2}{R} \times t$

$$\Rightarrow \frac{t_1}{R_1} = \frac{t_2}{R_2} \Rightarrow \frac{6}{R_1} = \frac{8}{R_2} \Rightarrow \frac{R_1}{R_2} = \frac{3}{4}$$

51. (4) Clearly, 2Ω , 4Ω and $(1 + 5) \Omega$ resistors are in parallel.

Hence, potential difference is same across each of them.


$$\therefore I_1 \times 2 = I_2 \times 4 = I_3 \times 6$$

Given $I_1 = 3A$ $\therefore I_1 \times 2 = I_3 \times 6$

Given $I_1 = 3A$.

$$\therefore I_1 \times 2 = I_3 \times 6 \text{ provides}$$
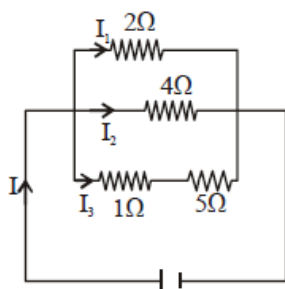
$$I_3 = \frac{I_1 \times 2}{6} = \frac{3 \times 2}{6} = 1A$$



Now, the potential across the 5Ω resistor is

$$V = I_3 \times 5 = 1 \times 5 = 5V.$$

\therefore The power dissipated in the 5Ω resistor

$$P = \frac{V^2}{R} = \frac{5^2}{5} = 5 \text{ watt}$$

52. (2) $P = Vi = \frac{V^2}{R}$

$$R_{\text{hot}} = \frac{V^2}{P} = \frac{200 \times 200}{100} = 400 \Omega$$


$$R_{\text{cold}} = \frac{400}{10} = 40 \Omega$$

53. (2) Let ρ be resistivity of the material of the wire and r be radius of the wire. Therefore, resistance of l m wire

$$R = \frac{\rho(1)}{\pi r^2} = \frac{\rho}{\pi r^2} \quad \left(\because R = \frac{\rho l}{A} \right)$$

Let ϵ be emf of each cell.

In first case,

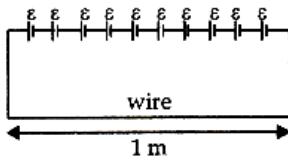


10 cells each of emf ϵ are connected in series to heat the wire of length 1 m by $\Delta T (= 10^\circ\text{C})$ in time t .

$$\therefore \frac{(10\epsilon)^2}{R} t = ms\Delta T \quad \dots(i)$$

In second case,

Resistance of same wire of length 2 m is
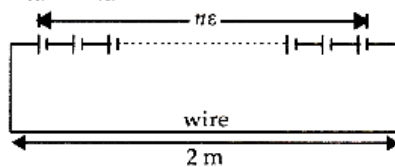
$$R' = \frac{\rho(2)}{\pi r^2} = \frac{2\rho}{\pi r^2} = 2R$$



Let n cells each of emf ϵ are connected in series to heat the same wire of length 2 m, by the same temperature $\Delta T (= 10^\circ\text{C})$ in time same time t .

$$\therefore \frac{(n\epsilon)^2 t}{2R} = (2m)s\Delta T \quad \dots(ii)$$

Divide (ii) by (i), we get

$$\frac{n^2}{200} = 2 \Rightarrow n^2 = 400 \quad \therefore n = 20$$

54. (1) Power $\propto \frac{1}{\text{Resistance}}$

In series combination, resistance doubles. Hence, power will be halved.

In parallel combination, resistance halves. Hence, power will be doubled.

55. (2) $\frac{R_1}{R_2} = \frac{V^2/P_1}{V^2/P_2} = \frac{P_2}{P_1}$

$$= \frac{\rho l / \pi (d_1/2)^2}{\rho l / \pi (d_2/2)^2} = \frac{d_2^2}{d_1^2} = \frac{100\text{W}}{25\text{W}} \Rightarrow \frac{d_2}{d_1} = \frac{10}{5} = \frac{2}{1}$$

56. (2) $H = \frac{V^2}{R} \times 15 \times 60 = \frac{V^2}{(2/3)R} \times t$

or $t = \frac{2}{3} \times 15 \times 60 = 600\text{s} = 10 \text{ minutes}$

57. (3) $\frac{R_1}{R_2} = \frac{\ell_1}{\ell_2}$ where $\ell_2 = 100 - \ell_1$

In the first case $\frac{X}{Y} = \frac{20}{80}$

In the second case

$$\frac{4X}{Y} = \frac{\ell}{100 - \ell} \Rightarrow \ell = 50$$

58. (3) Potential Gradient (x) = Potential drop per unit length $x = \frac{V}{l}$

V = Potential Difference

$$L = \text{length.} \Rightarrow R = \frac{\rho l}{A}$$

ρ = specific resistance

A = Area

$$x = \frac{ir}{l} = \frac{i\rho l}{la} = \frac{i\rho}{l}$$

$$x = \frac{0.2 \times 4 \times 10^{-7}}{8 \times 10^{-7}} = 0.1 \text{ units}$$

59. (1) We know

$$\frac{I}{I_s} = 1 + \frac{G}{S} \Rightarrow \frac{750}{100} = 1 + \frac{13}{S} \Rightarrow S = 2\Omega$$

60. (4) In balance condition, since no current flows through the galvanometer therefore B and D are at the same potential.

61. (1) It is a balanced Wheatstone bridge $\left(\because \frac{3}{4} = \frac{6}{8}\right)$, so the 7Ω resistance is ineffective.

Equivalent resistance of 3Ω and $4\Omega = 3 + 4 = 7\Omega$ (series)

Equivalent resistance of 6Ω and $8\Omega = 6 + 8 = 14\Omega$ (series)

Equivalent resistance of 7Ω and 14Ω (parallel)

$$= \frac{7 \times 14}{7 + 14} = \frac{14}{3}\Omega$$

62. (1) Due to increases in resistance R the current through the wire will decrease and hence the potential gradient also decreases, which results in increase in balancing length. So, J will shift towards B .

63. (2) $r = \frac{\ell_1 - \ell_2}{\ell_2} \times R\Omega$


Here, $\ell_1 = 125\text{cm}$, $\ell_2 = 100\text{cm}$, $R = 2\Omega$

$$\therefore r = 0.5\Omega$$

64. (2) $E_1 \propto 64$ $E_1 - E_2 \propto 8$ $E_2 \propto l$

$$\therefore 64 - l = 8 \text{ or } l = 64 - 8 = 56\text{cm}$$

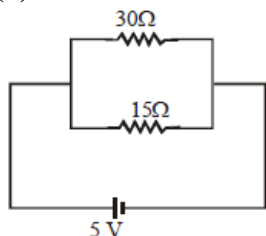65. (2) The network of resistors is a balanced Wheatstone bridge. The equivalent current is




$$R_{eq} = \frac{15 \times 30}{15 + 30} = 10\Omega$$

$$\Rightarrow I = \frac{V}{R} = \frac{5}{10} = 0.5A$$

NEET PREVIOUS YEARS QUESTIONS-EXPLANATIONS

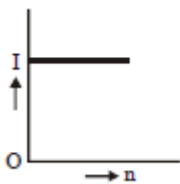1. (1) Short circuited current, $I = \frac{n\varepsilon}{nr} = \frac{\varepsilon}{r}$



So, I is independent of n and I is constant.

2. (1) In series grouping equivalent resistance $R_{\text{series}} = nR$
In parallel grouping equivalent resistance

$$R_{\text{parallel}} = \frac{R}{n}; I = \frac{E}{nR + R} \text{-----(i)}$$

$$10I = \frac{E}{\frac{R}{n} + R} \text{-----(ii)}$$

Dividing eq. (ii) by (i),

$$10 = \frac{(n+1)R}{\left(\frac{1}{n} + 1\right)R}$$

Solving we get, $n = 10$

3. (2)

4. (2) We know that, $R = \frac{\rho l}{A}$ or $R = \frac{\rho l^2}{\text{Volume}} \Rightarrow R \propto l^2$

According to question $l_2 = n l_1$

$$\frac{R_2}{R_1} = \frac{n^2 l_1^2}{l_1^2} \text{ or } \frac{R_2}{R_1} = n^2 \Rightarrow R_2 = n^2 R_1$$

5. (2) Reading of potentiometer is accurate because during taking reading it does not draw any current from the circuit.
6. (4) When two cells are connected in series i.e., $E_1 + E_2$ the balance point is at 50 cm. And when two cells are connected in opposite direction i.e., $E_1 - E_2$ the balance point is at 10 cm. According to principle of potential

$$\frac{E_1 + E_2}{E_1 - E_2} = \frac{50}{10} \Rightarrow \frac{2E_1}{2E_2} = \frac{50+10}{50-10} \Rightarrow \frac{E_1}{E_2} = \frac{3}{2}$$

7. (1) **Given:** Charge $Q = at - bt^2$

$$\therefore \text{Current } i = \frac{\partial Q}{\partial t} = a - 2bt \quad \left\{ \text{for } i = 0 \Rightarrow t = \frac{a}{2b} \right\}$$

From joule's law of heating, heat produced $dH = i^2 R dt$


$$H = \int_0^{\frac{a}{2b}} (a - 2bt)^2 R dt = \frac{(a - 2bt)^3}{-3 \times 2b} \Bigg|_0^{\frac{a}{2b}} = \frac{a^3 R}{6b}$$

8. (4)

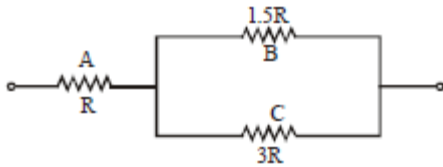9. (4) Effective resistance of B and


$$= \frac{R_B \cdot R_C}{R_B + R_C} = \frac{1.5R \times 3R}{1.5R + 3R} = \frac{4.5R^2}{4.5R} = R$$

i.e., equal to resistance of voltmeter A.



In parallel potential difference is same so,
 $V_B = V_C$ and in series current is same
 So, $V_A = V_B = V_C$

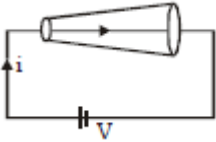
10. (1) Here, metallic conductor can be considered as the combination of various conductors connected in series. And in series combination current remains same.




11. (2) This is a balanced Wheatstone bridge condition,

$$\frac{5}{R} = \frac{l_1}{100 - l_1} \text{ and } \frac{5}{R/2} = \frac{1.6l_1}{100 - 1.6l_1} \Rightarrow R = 15\Omega$$

- 12.

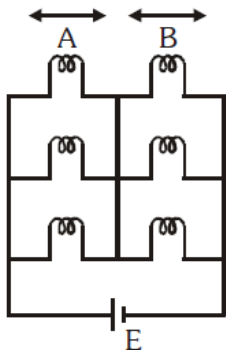

Case-I

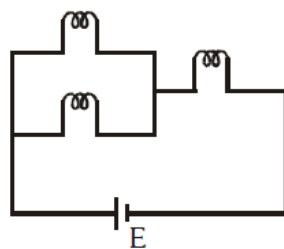

Case-II

$$R_{eq1} = 2R/3$$

$$P_{eq1} = \frac{E^2}{2R/3} = \frac{3P}{2}$$


$$\therefore P_{eq1} : P_{eq2} = 9 : 4$$

$$R_{eq2} = R/2 + R = \frac{3R}{2}$$


$$P_{eq2} = \frac{E^2}{3R/2} = \frac{2P}{3}$$

13. Fuse is used for protection

- 14.

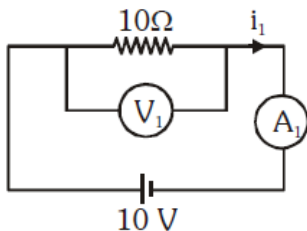

Circuit 1

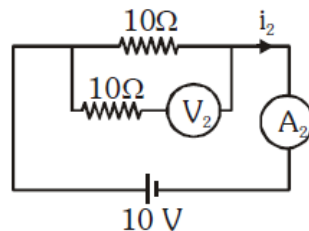

Circuit 2

10Ω is in series with ideal voltmeter. Therefore it will not affect the circuit (Circuit-2)

$$i_1 = 10/10 = 1A ; i_2 = 10/10 = 1A$$

$$V_1 = 10V ; V_2 = 10V$$

15. **Concept based**

16.
$$\frac{E_1}{E_2} = \frac{\phi l_1}{\phi l_2} ; \frac{1.5}{2.5} = \frac{36}{l_2}$$

$$\Rightarrow l_2 = 36 \times \frac{5}{3} = 60\text{cm}$$

17. $I = \frac{2+4}{4+1+1} = \frac{6\text{V}}{6\Omega} = 1\text{A}$

18. Resistance of conductor, $R = \frac{\rho l}{A} \Rightarrow A = \frac{\rho l}{R}$

$$\Rightarrow \frac{A_1}{A_2} = \frac{\rho_1}{\rho_2} \times \frac{l_1}{l_2} \times \left(\frac{R_2}{R_1}\right) = 1$$


[$\because R_1 = R_2, l_1 = l_2$ and for same material $\rho_1 = \rho_2$]

19. By KVL


$$-I_1 R_2 - E_2 + E_3 + I_3 R_1 = 0$$

$$\Rightarrow I_2 R_2 + E_2 - E_3 - I_3 R_1 = 0$$


20.

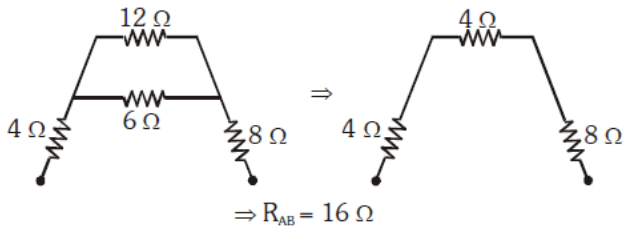

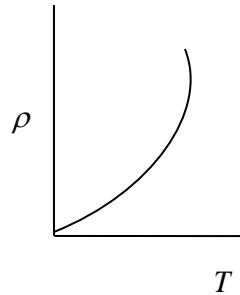21. The variation of resistivity of copper with temperature is parabolic in nature



22.

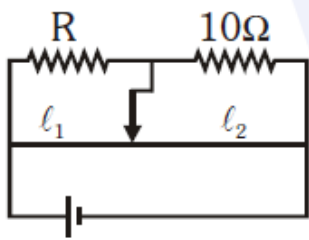

$$\frac{R}{l_1} = \frac{10}{l_2}$$

$$R = \frac{3}{2} \times 10$$

$$R = 15\Omega$$

Given length of R is 1.5 m

length of 10Ω is

$$l = 1 \times 10^{-1} \text{m}$$

23. Mobility $\mu = \frac{V_d}{E} = \frac{7.5 \times 10^{-4}}{3 \times 10^{-10}} = 2.5 \times 10^6 \text{m}^2 \text{V}^{-1} \text{S}^{-1}$

24. Yellow - 4
Violet - 7

Brown - 10

Gold = 5%

$$R = 47 \times 10 \pm 5\% = 470 \pm 5\% \Omega$$

25. When temperature increases, free electron density increases for semiconductors and insulators
Temperature coefficient of resistance is negative for semiconductors and insulators

26. $V_d = a\tau = \frac{Ee}{m} \tau$ $j = \frac{i}{A} = nev_d$

$$P = \frac{E}{J} \qquad \tau = \frac{m}{ne^2 P}$$

27. $\frac{E_2}{E_1} = \frac{l_2}{l_1} \Rightarrow \frac{2.5}{1.5} = \frac{l_2}{36} \Rightarrow l_2 = 60 \text{ cm}$

$$R_p = \frac{R}{n} = 0.25 \Omega$$


28.

$$\Rightarrow \frac{R}{4} = 0.25 \Omega$$

$$\Rightarrow R = 1 \Omega$$

$$R_s = nR = 4 \times 1 = 4 \Omega$$

29.

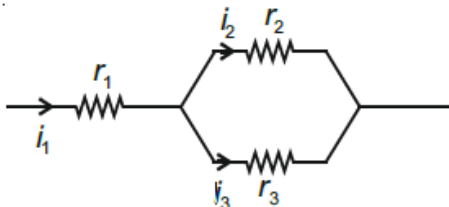

In parallel combination of resistances r_2 and r_3 , potential difference will be equal across both resistance.

$$\text{So, } i_2 r_2 = i_3 r_3 \Rightarrow i_2 = \frac{i_3 r_3}{r_2} \dots \dots \dots (1)$$

As per Kirchhoff's first law

$$\Rightarrow i_1 = i_2 + i_3$$

$$\Rightarrow i_1 = \left(\frac{r_3}{r_2} + 1 \right) i_3 \quad (\text{from equation 1})$$

$$\Rightarrow \frac{i_3}{i_1} = \frac{r_2}{r_2 + r_3}$$

30. $R = \frac{\rho L}{A} \Rightarrow \rho = \frac{RA}{L}$

$$J = \sigma E = \frac{E}{\rho} = \frac{EL}{RA}$$

$$J = \frac{10 \times 10}{10 \times \pi \left[\frac{10^{-2}}{\sqrt{\pi}} \right]^2} = 10^5 \text{ A/m}^2$$

31. $\theta = \frac{V^2}{R}$

$$\frac{Q_1}{Q_2} = \frac{R_2}{R_1} = \frac{200}{100} = 2$$

32. The value of X can be more precisely measured if the resistances P and Q approximately equal and small.